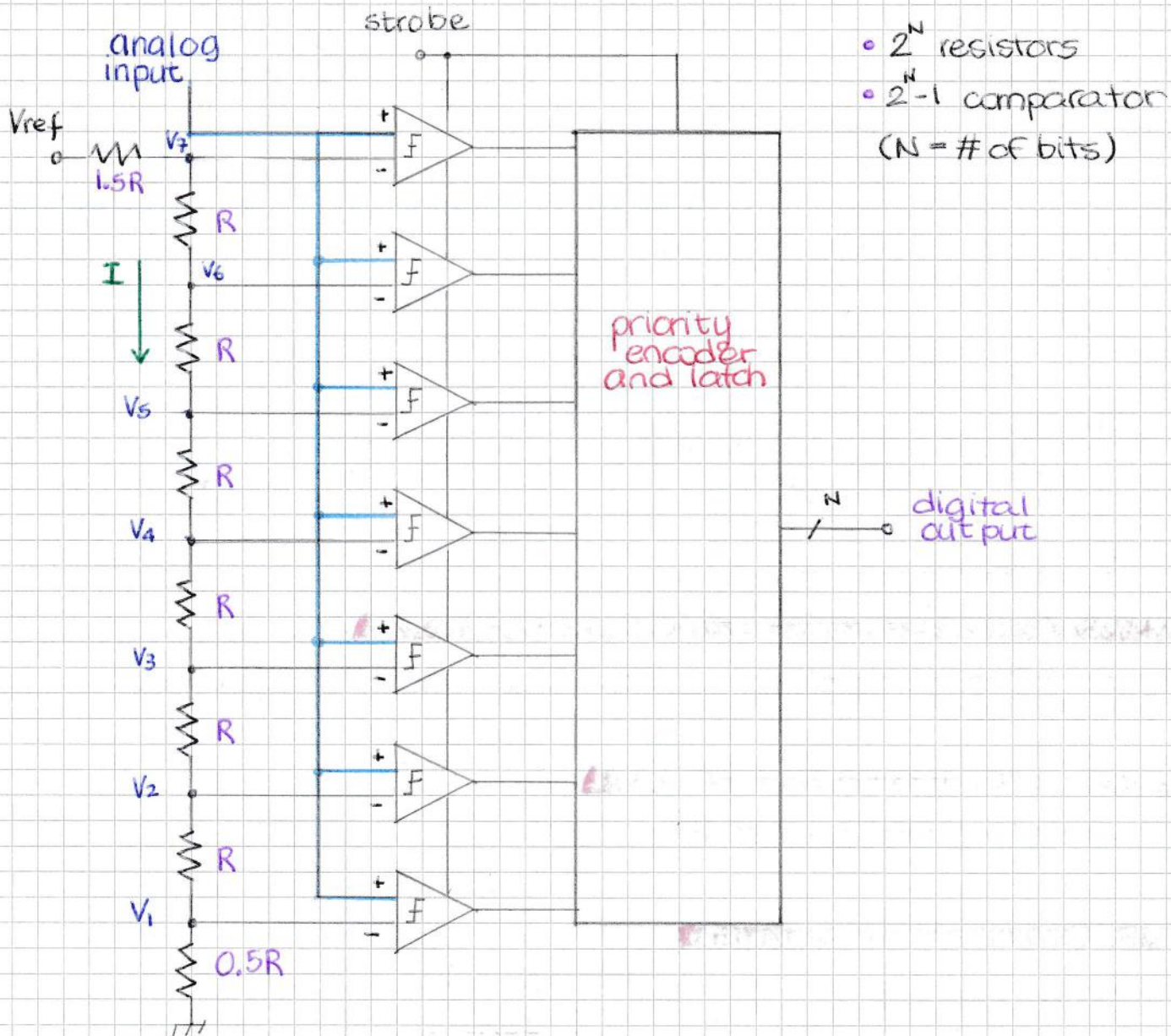


# FLASH CONVERTER

(Saletti)

02/11

- parallel ADC
  - bit computed at same time
  - fastest way to convert
- large bandwidth
- high power consumption
- expensive
- low resolution
- occupies more space



$$R_{eq} = 1.5R + 6R + 0.5R = 8R \quad (\text{series of resistors})$$

$$I = V_{ref} / 8R \Rightarrow \text{current flowing through the "ladder"}$$

$$V_1 = I \cdot \frac{1}{2}R = \frac{V_{ref}}{16}$$

$$V_2 = (R + \frac{1}{2}R) \cdot I = \frac{3}{16} V_{ref}$$


these values get compared with the analog input signal

if  $V_i < V_{input} \Rightarrow \text{out} = 1$

← equally spaced

 ⇒ the input signal is compared with every step of the ladder. in output (from the bottom) we have a series of "1" until a voltage is found that is higher than input signal so the comparator output is 0





• output of converter generated by selecting the top "1" in the set of threshold

find which is the last threshold that is smaller than  $V_{in}$


next threshold will be  $> V_{in}$

**PRIORITY ENCODER:** selects the last "step"  $< V_{in}$

## SUCCESSIVE - APPROXIMATION ADC (SAR)

- most popular for data-acquisition applications
- resolution: 8 ÷ 18 bits
- sampling rate: up to several MHz (slower than flash ADC)
- output generally provided with serial interface
- typically provided with **sample & hold circuit** to "freeze" input signal during conversion

### successive approximation

 


- 1) first bit = 1
- 2) if  $V_{in} > V_{DAC}$  next step  
else first bit is changed to 0
- 3) successive bit = 1

conversion is over after  $N$  steps ( $N$  = resolution)


since it takes time to convert value into  $V_{DAC}$  and compare  $V_{in}$  must be constant (**sample and hold**)

### architecture

 



## Timing

 


## NOTE

- binary-tree-research alike conversion algorithm
- internal DAC set to midscale
 
## TWO-STAGE SUBRANGING ADC (ex: 6bit converter)

two stages = 2 conversions { one coarse for 1<sup>st</sup> half  
one finer for 2<sup>nd</sup> half



1<sup>st</sup> stage


↳ coarse (first 3b)

2<sup>nd</sup> stage

↳ fine (other 3b)

- 1) finds value closest to  $V_{in}$  (3)
- 2) this value goes into a DAC
- 3) calculate  $V_{in} - V_{DAC}$
- 4) difference is amplified between 0 and  $V_{ref}$
- 5) convert the residual signal with 3 bits


## ARCHITECTURE

 





- sample and hold: "freezes" signal during conversion
- $2 \times 2^{N/2} - 1$  comparators needed (vs  $2^N - 1$  in single stage)
- less area and dissipated power (+)
- lower conversion rate (-)

## PIPELINE ADC

 

- at every time each stage of the converter operates on a different input value
- less time for conversion (+)
- to convert a single value it takes  $N$  clock cycle with  $N$  being the number of different stages (-)

## DUAL SLOPE ADC

 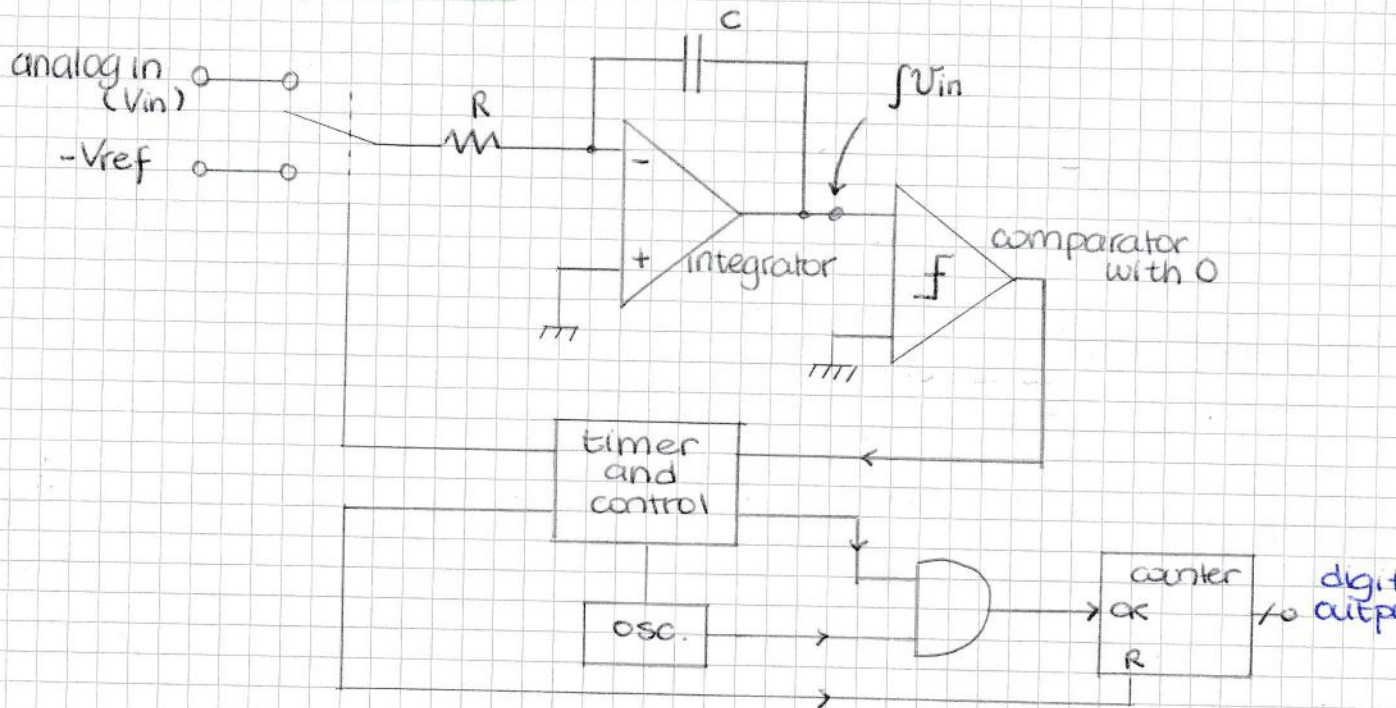

1)  $V_{in}$  is integrated for a known time  $T$

↳ the 1<sup>st</sup> slope depends on the value of  $V_{in}$

2) switch goes from  $V_{in} \rightarrow -V_{ref}$


3)  $-V_{ref}$  gets integrated  $\rightarrow$  constant negative slope

4) after an unknown time  $t_x$  the value reaches 0 and the computation ends

$t_x$  depends on the point reached by the first slope and it gets measured by the counter

$$t_x = \frac{V_{in}}{V_{ref}} \cdot T$$

## noise effect

 

with sample and hold we may "freeze" at the wrong time (when noise is bigger compared to  $V_{in}$ )


↓  
we're integrating on the entire period of the NOISE itself so the NOISE gets canceled

$\Rightarrow$  integral calculation smooths down noise effect


 
# PRINCIPLE OF OVERSAMPLING

sampling input signal at a frequency much larger than the required one ( $K \cdot f_s$ )



→ without oversampling: quantization noise always present between  $0$  and  $f_s/2$

→ with oversampling: quantization noise is spread between  $0$  and  $K \cdot f_s/2$

→ by filtering out frequencies  $> Kf_s/2$  the noise is largely reduced

**GAIN** = 3dB for each doubling of  $K$

**DECIMATION (DEC)**: we have way more samples than needed, this filter takes 1 sample every  $K$

↳ must operate at a  $K$  times higher frequency


(+) noise reduction

(-) DEC filter must operate at high frequency


} need to find a balance when choosing  $K$
 
## $\Sigma - \Delta$ ADC BASIC PRINCIPLES


oversampling with  $\Sigma - \Delta$  modulator to change the shape of noise by "pushing" it towards higher frequencies



 when filtering high frequencies we remove more noise than before



## architecture

 


• modulator output = 1bit stream

• quantization noise shaped towards high frequency



 
a)  $V_{in} = 0$

- integrator receives  $0 + V_{ref} = V_{ref}$  and then  $0 - V_{ref} = -V_{ref}$
- integrator output = positive or negative ramp
- comparator gives 1 or 0 according to the ramp sign
- each time the sign of  $V_{ref}$  changes so the signal that gets integrated changes sign too



 b)  $V_{in} = V_{ref}/2$

- integrator receives  $V_{ref} + V_{ref}/2 = 3V_{ref}/2$   
 $V_{ref}/2 - V_{ref} = -V_{ref}/2$
- slope less steep than before, it takes 3 clocks to change from 1  $\rightarrow$  0



- the number of "1" gives us information about  $V_{in}$
- one result every interval decimates the oversampled sequence

a)  $V_{in} = 0$

output seq: 0-1-0-1-0-1-0-1...  $\Rightarrow$  8 "1"s over 16 samples  
 1 output every 16 samples  $\Rightarrow$  output = 1000

b)  $V_{in} = V_{ref}/2$

output seq: 0-1-1-1-0-1-1-1...  $\Rightarrow$  12 "1"s over 16 samples  
 1 output every 16 samples  $\Rightarrow$  output = 1100

- (+) operations on 1 bit (simpler)
- (+) fast, can oversample more, reducing noise even more



## 2<sup>nd</sup> ORDER $\Sigma$ - $\Delta$ MODULATOR

- adds one integrator before the other one
- both get  $V_{in} - V_{DAC}$  as input
- (+) further improvement of SNR


## $\Sigma$ - $\Delta$ PROS AND CONS

- (+) less noise
- (+) 1 bit architecture
- (+) most of computation is made on digital
- (-) oversampling requires high clock frequencies
- (-) filtering takes several cycles causing latency between input and output

## DIGITAL TO ANALOG CONVERTERS (DAC)

typically used in motor control, we need to generate a voltage (or current) from sequences of bits

## BINARY WEIGHTED RESISTORS

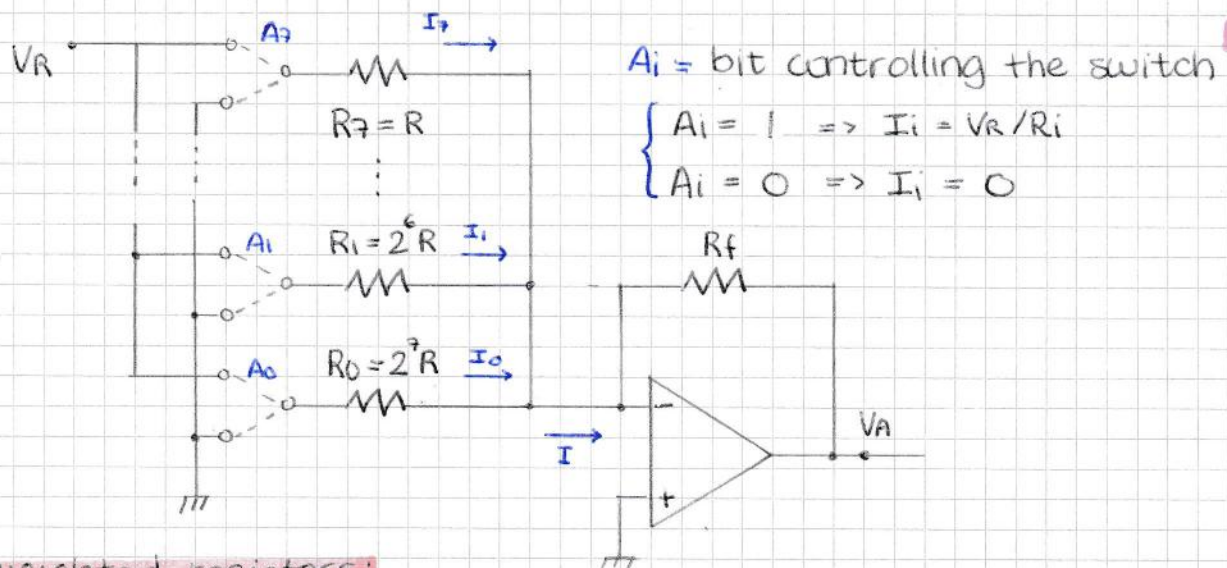

## weighted resistors:


if the bit is more significative the current of the corresponding branch is bigger

ex:  $I_7 = V_R / R$ ;  $I_0 = V_R / 2^7 R$


- (-) different values of resistors
  - (+) simple architecture
- } good with low resolutions



# R-2R LADDER RESISTORS

 

## equivalent circuit

 

bits "control" voltage generators

$V_{TH}$  (MSB  $\rightarrow$  rightmost generator)

$$V_{TH} = \frac{V_R}{2}$$

$V_{TH}$  (LSB  $\rightarrow$  leftmost generator)


$$V_{TH} = \frac{V_R}{16} \rightarrow \text{at each "step" } V_R \text{ is divided by 2}$$

the position of each generator determines its effect on the final voltage

each bit has its own weight


 
## DIFFERENZA TRA SAMPLE AND HOLD (S/H) E TRACK AND HOLD (T/H)



Entrambi i tipi di circuiti campionano il segnale di ingresso e mantengono costante la tensione campionata per la durata del processo di conversione. L'uscita del circuito T/H (a destra) traccia il segnale di ingresso finché non viene segnalato di effettuare il campionamento, quindi mantiene il valore di campionamento durante la conversione ADC. Il circuito S/H ha un'apertura di campionamento più breve e la sua uscita è una serie di livelli campionati (a sinistra). La differenza chiave tra T/H e S/H è la durata dell'intervallo di tracciamento: molto breve nel caso di S/H e molto più lunga nel caso di T/H. Entrambi i circuiti si basano su un commutatore veloce per isolare un condensatore di immagazzinaggio che è stato collegato all'ingresso del segnale