



Electronics Systems (938II)

Lecture 3.6

Semiconductor Memories – DRAM, SDRAM, and DDR

RAM – Reminder


- RAM classification
 - **Static RAM (SRAM)**
 - The memory content is hold over the time, as long as the memory is powered
 - **Dynamic RAM (DRAM)**
 - Even if the memory is powered, the memory content needs to be refreshed over the time, otherwise it is lost

RAM – Reminder

- RAM classification
 - **Static RAM (SRAM)**
 - The memory content is hold over the time, as long as the memory is powered
 - **Dynamic RAM (DRAM)**
 - Even if the memory is powered, the memory content needs to be refreshed over the time, otherwise it is lost


DRAM – Memory cell

- Capacitor

 


DRAM – Memory cell

 - Capacitor
 - **Memory bit = Voltage on capacitor (V_C)**




DRAM – Memory cell

 - Capacitor
 - Memory bit = Voltage on capacitor (V_C)



 
$$V_C = \begin{cases} V_{CC} & (\text{logic } 1) \\ 0 & (\text{logic } 0) \end{cases}$$




DRAM – Memory cell

 - Architecture
 - Capacitor
 - 1x access transistor
- WL_i = Word Line
- BL_j = Bit Line



DRAM – Memory cell

- Working principle

 


DRAM – Memory cell

- Working principle

- Write

 - $WL_i = 1$
- $BL_i = D$
 - 0 V (logic 0)
 - V_{CC} (logic 1)




DRAM – Memory cell

- Working principle


- Write

 - $WL_i = 1$
- $BL_i = D$
 - 0 V (logic 0)
 - V_{CC} (logic 1)




DRAM – Memory cell

 - Working principle
 - **After write**
 - $WL_i = 0$
 - Assume 1 (V_{CC}) written in memory cell / on capacitor



DRAM – Memory cell

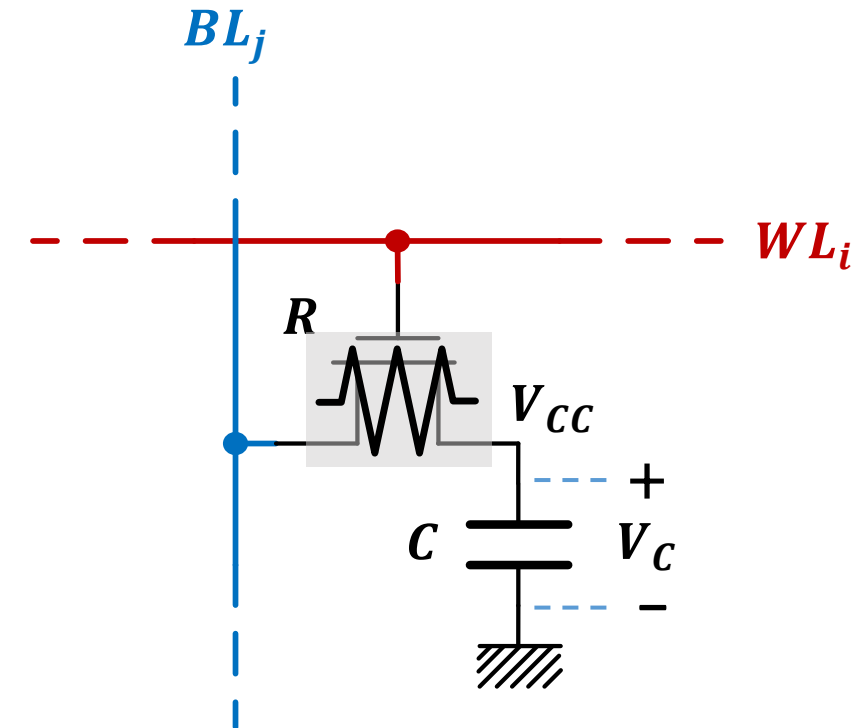- Working principle
 - **After write**
 - $WL_i = 0$
 - Assume 1 (V_{CC}) written in memory cell / on capacitor
 - **Access transistor \approx resistor (R)**
 - High impedance when $WL_i = 0$ (transistor OFF)




DRAM – Memory cell

- Working principle

- After write

 - $WL_i = 0$
 - Assume 1 (V_{CC}) written in memory cell / on capacitor
 - Access transistor \approx resistor (R)
 - High impedance when $WL_i = 0$ (transistor OFF)




DRAM – Memory cell

- Working principle

- After write

 - $WL_i = 0$
 - Assume 1 (V_{CC}) written in memory cell / on capacitor
 - Access transistor \approx resistor (R)
 - High impedance when $WL_i = 0$ (transistor OFF)
 - **Leakage (current, i) through capacitor dielectric**
 - Not ideal!




DRAM – Memory cell

- Working principle



- After write

 - $WL_i = 0$
 - Assume 1 (V_{CC}) written in memory cell / on capacitor
 - Access transistor \approx resistor (R)
 - High impedance when $WL_i = 0$ (transistor OFF)
 - Leakage (current, i) through capacitor dielectric
 - Not ideal!
 - C discharges!!!





DRAM – Memory cell

  - Working principle
 - After write
 - C discharges!!!





DRAM – Memory cell

  - Working principle
 - After write
 - C discharges!!!
 - Proportional to $R \cdot C = \tau$ (time constant)



DRAM – Memory cell

  - Working principle
 - After write
 - C discharges!!!
 - Proportional to $R \cdot C = \tau$ (time constant)
 - $\tau = 10 \div 100 \text{ ms}$



DRAM – Memory cell

- Working principle



- After write

- C discharges!!!

- Proportional to $R \cdot C = \tau$ (time constant)

- $\tau = 10 \div 100 \text{ ms}$

- Need of refresh

  

DRAM – Memory cell

- Working principle



- After write

- C discharges!!!

- Proportional to $R \cdot C = \tau$ (time constant)

- $\tau = 10 \div 100 \text{ ms}$

- Need of refresh

  

DRAM – Memory cell

- Working principle



- After write

- C discharges!!!

- Proportional to $R \cdot C = \tau$ (time constant)


- $\tau = 10 \div 100 \text{ ms}$

- Need of refresh

  

DRAM – Memory cell

- Working principle
 - Read

 


DRAM – Memory cell

- Working principle

- Read

- Step 1

 - $WL_i = 0$
 - $BL_j = \frac{V_{CC}}{2} = V_R$ (reading voltage)



DRAM – Memory cell

- Working principle

- Read


- Step 1

- $WL_i = 0$

- $BL_j = \frac{V_{CC}}{2} = V_R$

- Step 2

- $WL_i = 1$

 

DRAM – Memory cell

- Working principle


- Read

- Step 1

- $WL_i = 0$
 - $BL_j = \frac{V_{CC}}{2} = V_R$

- Step 2

 - $WL_i = 1$
 - $BL_j \approx C_{BL}$ (capacitor)
 - $C_{BL} \gg C$
 - V_{BL} = voltage on C_{BL}



DRAM – Memory cell

- Working principle

- Read


- Step 1

- $WL_i = 0$
- $BL_j = \frac{V_{CC}}{2} = V_R$

- Step 2

- $WL_i = 1$
- $BL_j \approx C_{BL}$ (capacitor)
 - $C_{BL} \gg C$
 - V_{BL} = voltage on C_{BL}

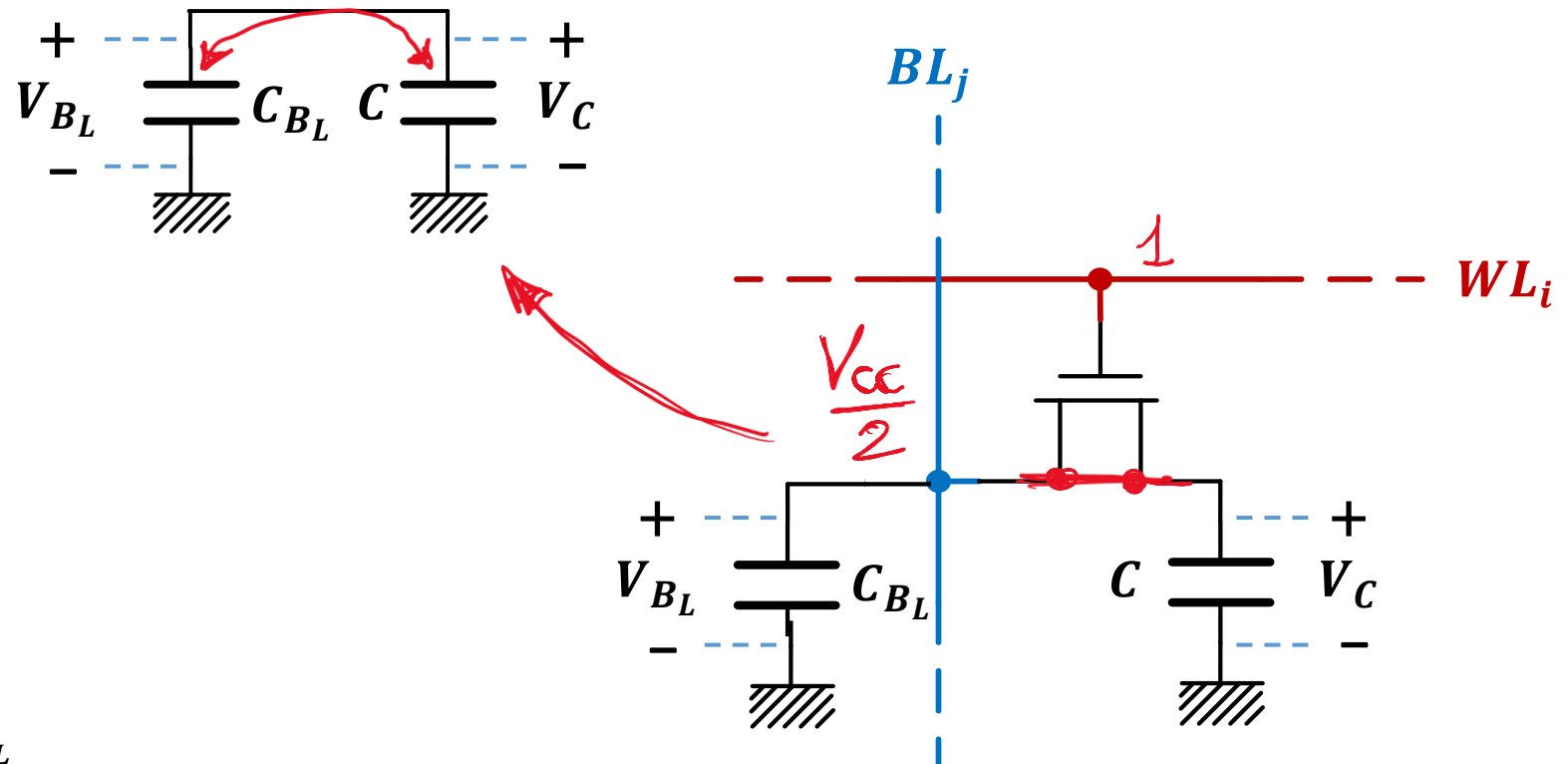- Charge redistribution between C_{BL} and C !




DRAM – Memory cell

- Working principle



- Read

- Charge redistribution!


 


- Read destroys data!
- Need of re-write!

Memory bit = 1 ($V_C = V_{CC}$)

  

Memory bit = 0 ($V_C = 0 V$)

  


DRAM – Memory cell

- Working principle



- Read

- Charge redistribution!


 


- Read destroys data!

Memory bit = 1 ($V_C = V_{CC}$)

  

Memory bit = 0 ($V_C = 0 V$)

  


DRAM – Memory cell

- Working principle



- Read

- Charge redistribution!


 


- Read destroys data!
- Need of re-write!

Memory bit = 1 ($V_C = V_{CC}$)

  

Memory bit = 0 ($V_C = 0 V$)

  

DRAM – Memory cell



- Working principle

- Read



- How to re-write?

- If $V_{BL} > V_R \rightarrow 1$
- If $V_{BL} < V_R \rightarrow 0$

Memory bit = 1 ($V_C = V_{CC}$)

  

Memory bit = 0 ($V_C = 0 V$)

  

DRAM – Memory cell

- Working principle

- Read



- How to re-write?

- If $V_{BL} > V_R \rightarrow 1$
- If $V_{BL} < V_R \rightarrow 0$



- $|V_{BL} - V_R|$

- Very small value
- Must be **amplified!**

Memory bit = 1 ($V_C = V_{CC}$)

  

Memory bit = 0 ($V_C = 0 V$)

  

DRAM – Memory cell

- Working principle

- Read

- How to re-write?



- If $V_{BL} > V_R \rightarrow 1$
- If $V_{BL} < V_R \rightarrow 0$

- $|V_{BL} - V_R|$



- Very small value
- Must be amplified!

- Sense Amplifier (SA)

Memory bit = 1 ($V_C = V_{CC}$)

  


Memory bit = 0 ($V_C = 0 V$)

  

DRAM – Architecture and working principle

- Draft
 - Sense Amplifier (SA)

 

DRAM – Architecture and working principle


- Draft

- Sense Amplifier (SA)

- How?

- **Bistable !**

- We have already seen in SRAM

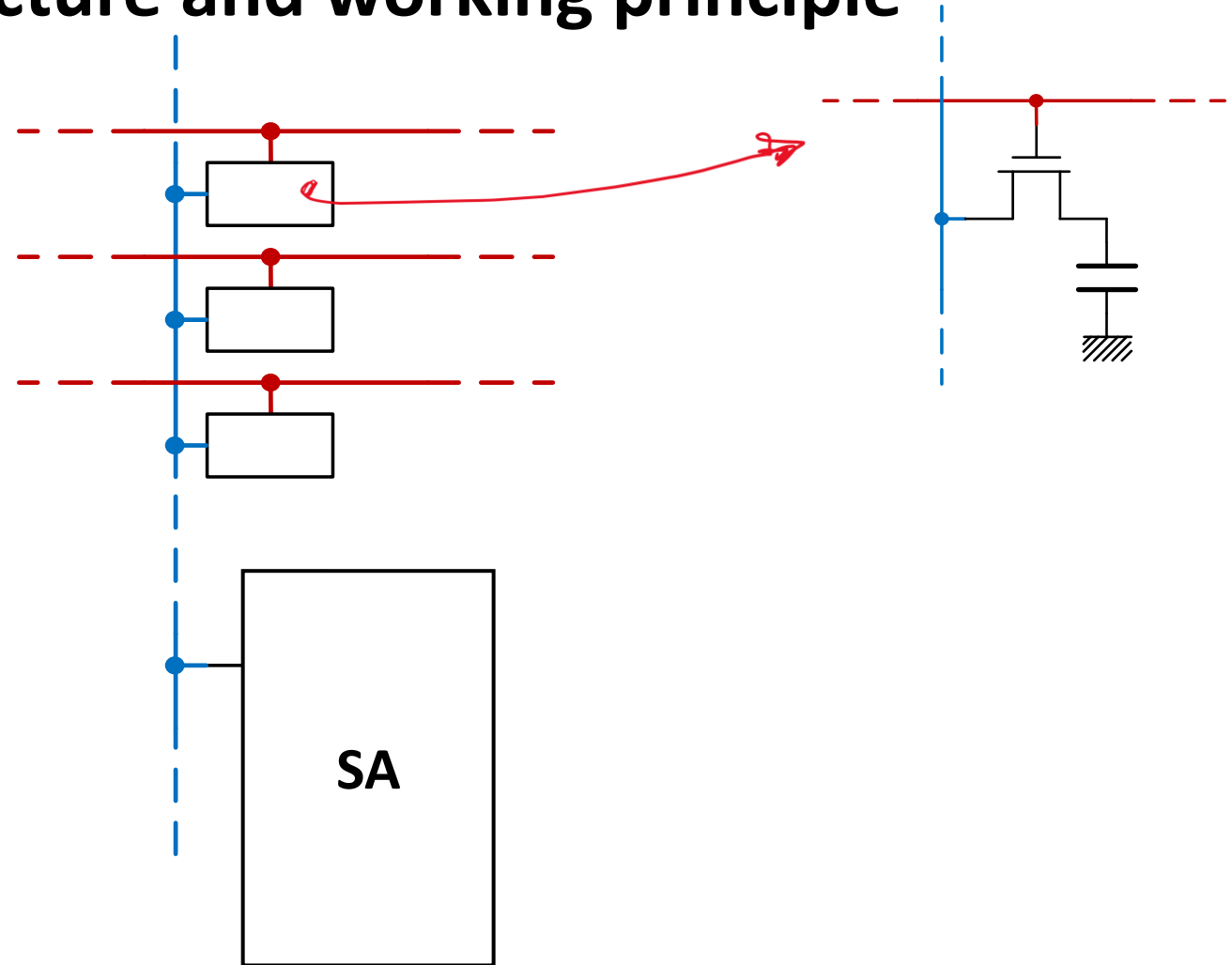

DRAM – Architecture and working principle


- Draft

- Sense Amplifier (SA)

- How?

- **Bistable !**

- We have already seen in SRAM

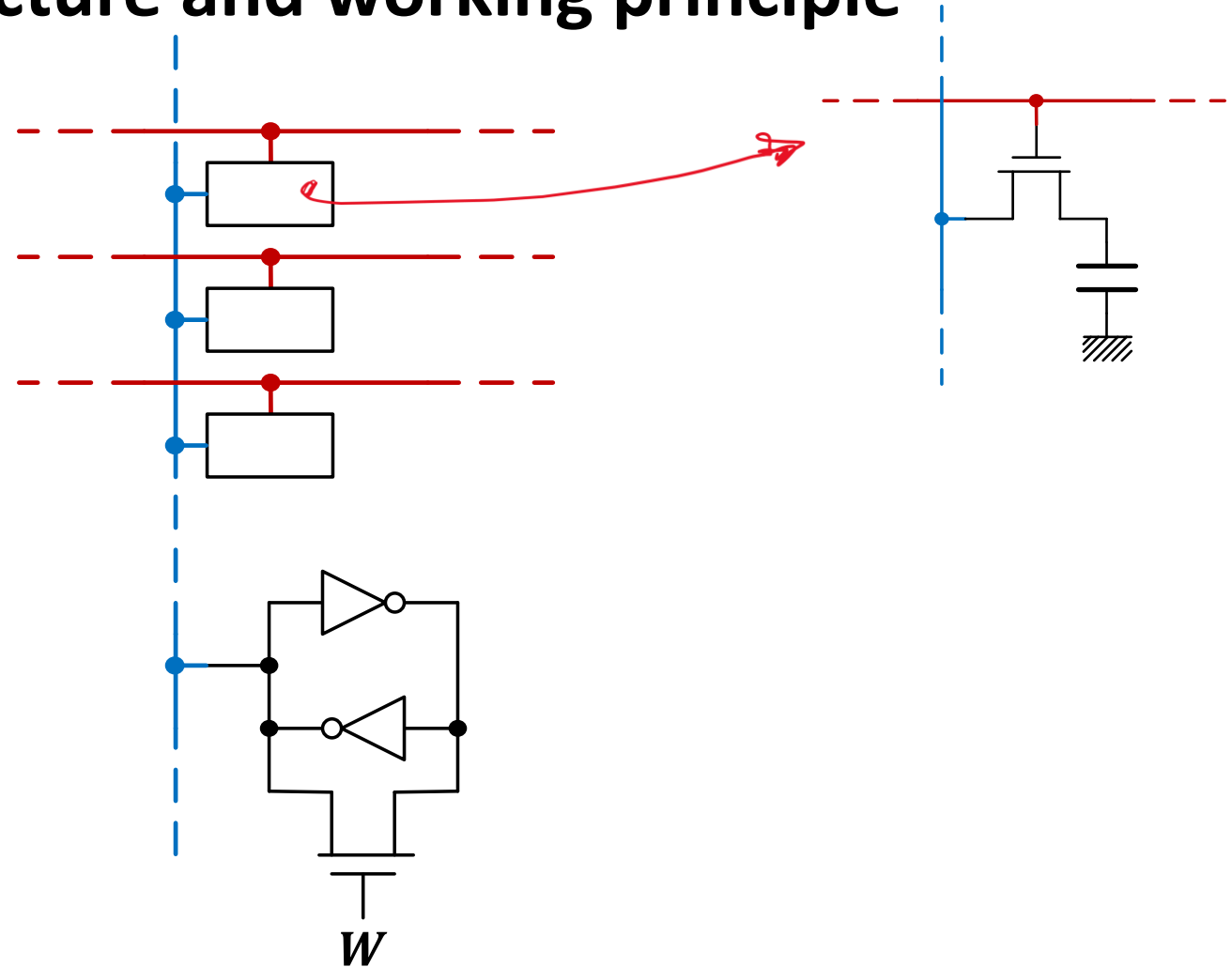


DRAM – Architecture and working principle

- Draft

- Sense Amplifier (SA)

- **Write** ($W = 1$)

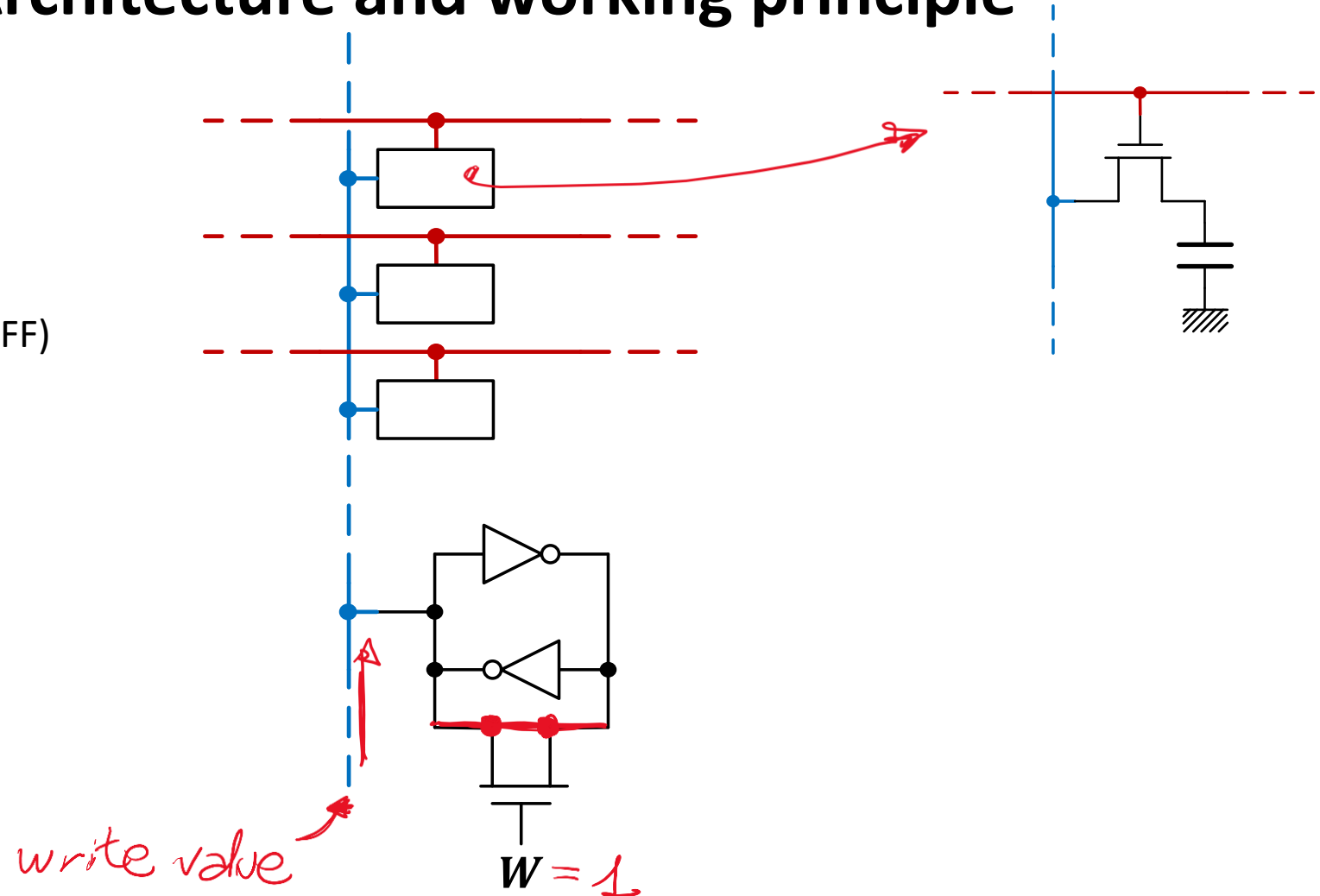- Bistable is bypassed (OFF)
 - Write value on Bit Line



DRAM – Architecture and working principle

- Draft


- Sense Amplifier (SA)

- Write ($W = 1$)

- Bistable is bypassed (OFF)
 - Write value on Bit Line

- Read ($W = 0$)

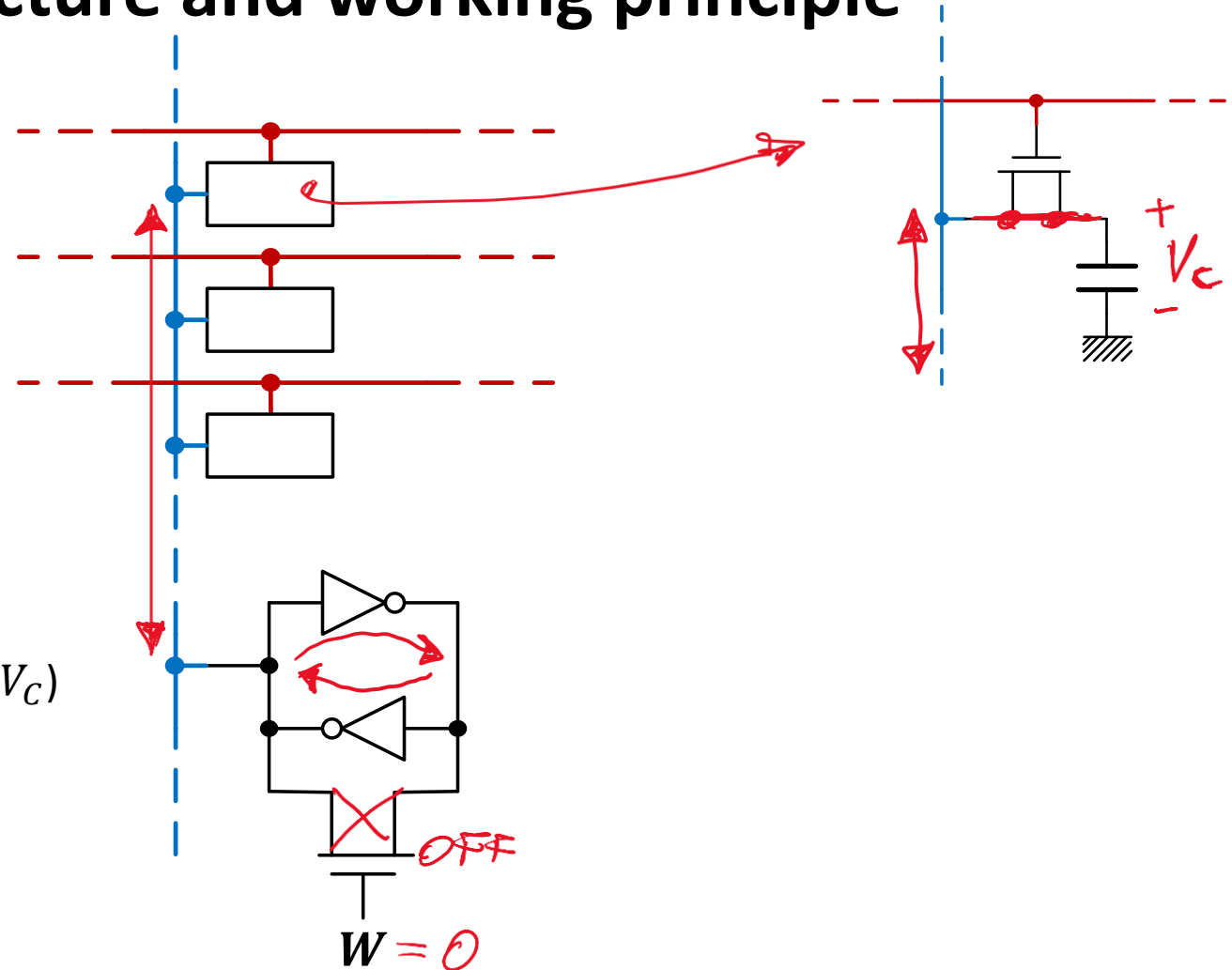- Bistable is ON
 - Bistable regenerates memory bit (V_C)




DRAM – Architecture and working principle

- Draft
 - Bit Lines are “big” capacitors (C_{BL})
 - SAs placed in the middle (of each BL) for balancing capacitive load (C_{BL})
 - In addition
 - SA block merged with the column-decoder for resource saving and architecture simplification


DRAM – Architecture and working principle

- Draft

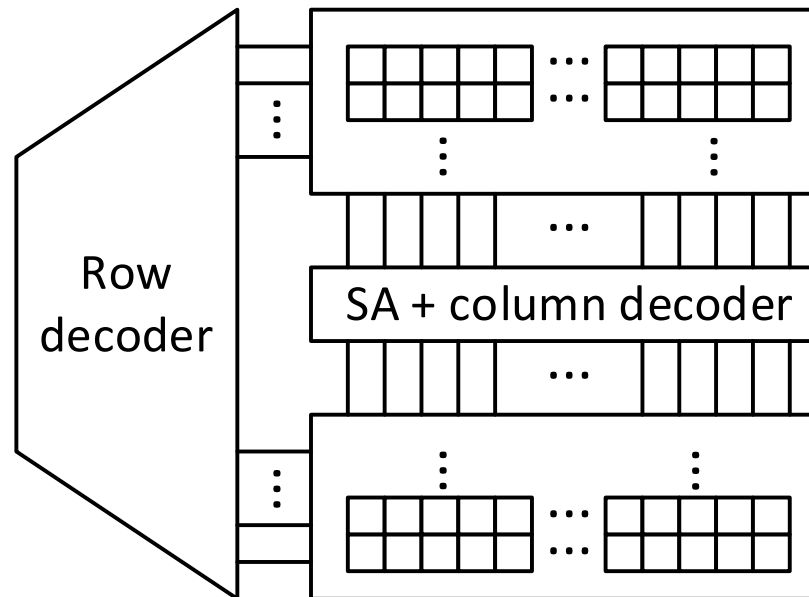


DRAM – Architecture and working principle

- Draft

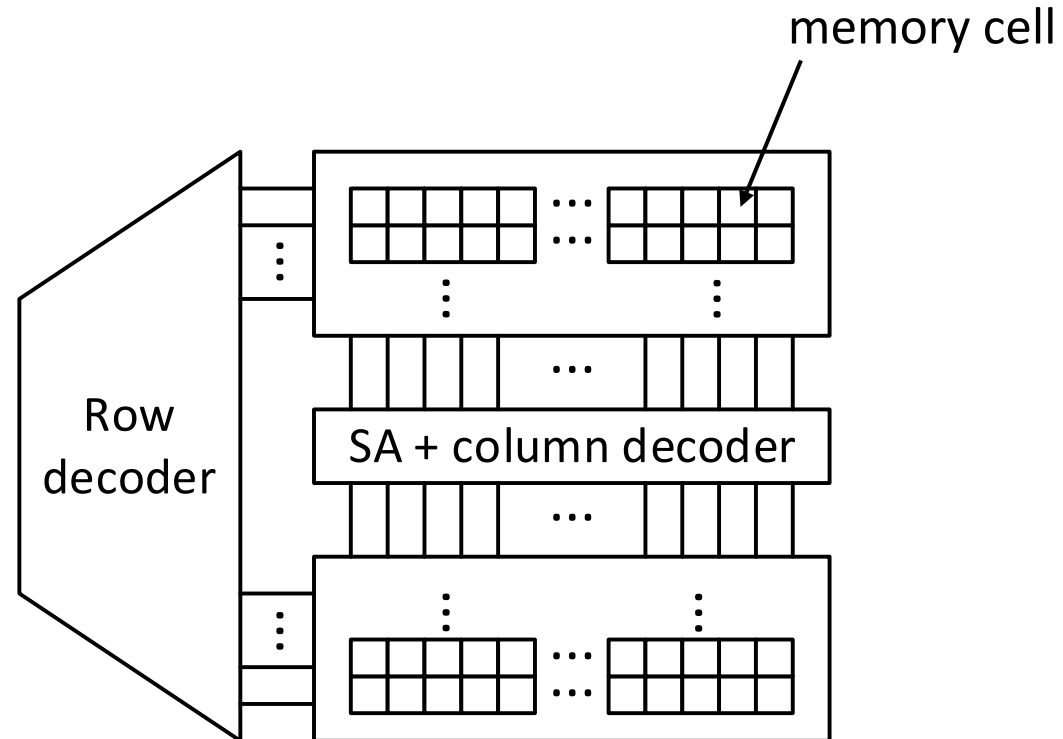


DRAM – Architecture and working principle

- Draft

 


DRAM – Architecture and working principle

 - Draft
 - Other problem(s)
 - When reading (or writing)
 - WL_i moves from 0 to 1




DRAM – Architecture and working principle

 - Draft
 - Other problem(s)
 - When reading (or writing)
 - WL_i moves from 0 to 1




DRAM – Architecture and working principle

 - Draft
 - Other problem(s)
 - When reading (or writing)
 - WL_i moves from 0 to 1
 - Capacitive coupling between WL_i and BL_j




DRAM – Architecture and working principle

 - Draft
 - Other problem(s)
 - When reading (or writing)
 - WL_i moves from 0 to 1
 - Capacitive coupling between WL_i and BL_j
 - To counteract this, the capacitive load seen by the SA must be balanced !




DRAM – Architecture and working principle

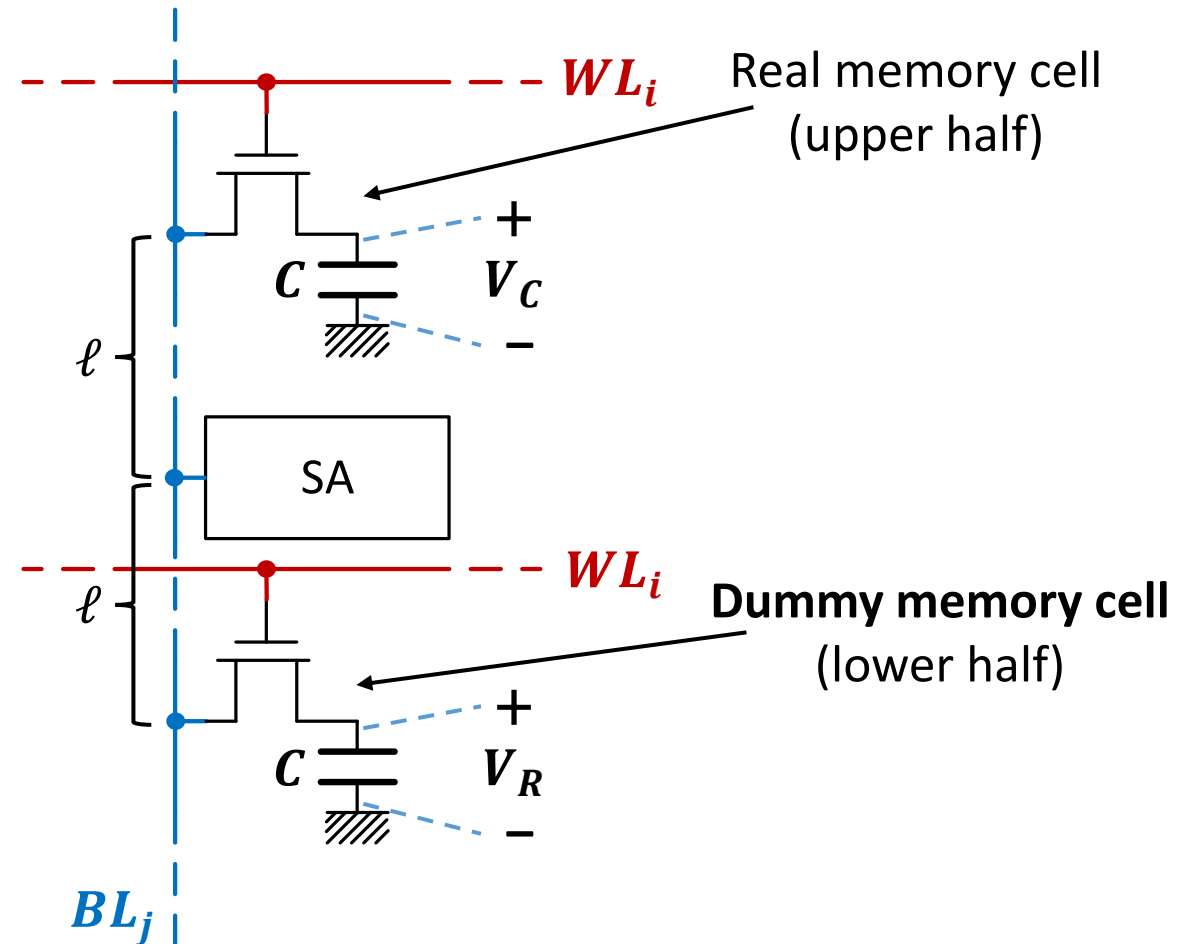- Draft
 - Balancing capacitive load seen by SA
 - Same distance ℓ in opposite directions
 - Same WL_i
 - Dummy memory cell
 - Opposite half
 - Preloaded at V_R




DRAM – Architecture and working principle

- Draft
 - Including dummy cells

 


DRAM – Architecture and working principle

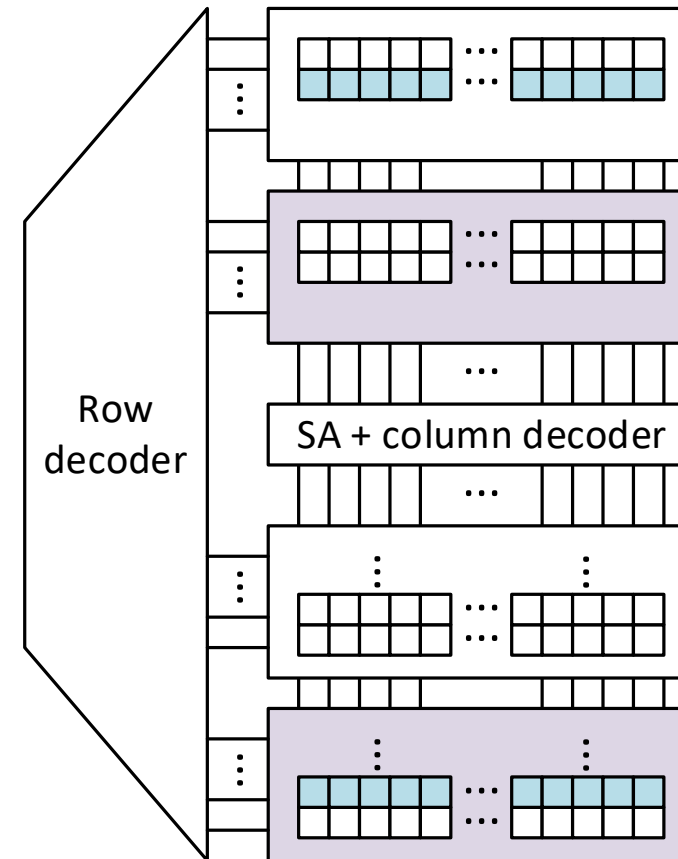- Draft
 - Including dummy cells
 - Example
 - Balancing **upper** half



DRAM – Architecture and working principle

 - Draft
 - Including dummy cells
 - Example
 - Balancing **lower** half



DRAM – Architecture and working principle

- Final
 - To complete the architecture, they should be integrated
 - Address
 - Write command/signal
 - Input data (D) and output data (Q) ports


DRAM – Architecture and working principle

- Final
 - To complete the architecture, they should be integrated
 - Address
 - Write command/signal
 - Input data (D) and output data (Q) ports
 - To reduce costs/save resources
 - Single I/O port
 - Single address port shared by row and column decoders
 - Buffer to store row/column address
 - **RAB** = **Row Address Buffer** ← triggered by signal **RAS** = **Row Address Strobe**
 - **CAB** = **Column Address Buffer** ← triggered by signal **CAS** = **Column Address Strobe**

DRAM – Architecture and working principle

- Final

 - A = address port
- Q = output (data) port
- D = input (data) port
- W = write command




DRAM – Architecture and working principle

- Memory bit stored inside the cells lasts at most 10 – 100 *ms*
 - **REFRESH** operation is required
 - Only row must be addressed to refresh the memory
 - All cells in the same row (Word Line) can be refreshed at the same time
 - T_{REF} = maximum time before refresh
 - Different approaches
 - Wait for T_{REF} and then refresh all memory rows
 - Wait for $\frac{T_{REF}}{\text{row number}}$ and refresh one row at a time


DRAM – Architecture and working principle

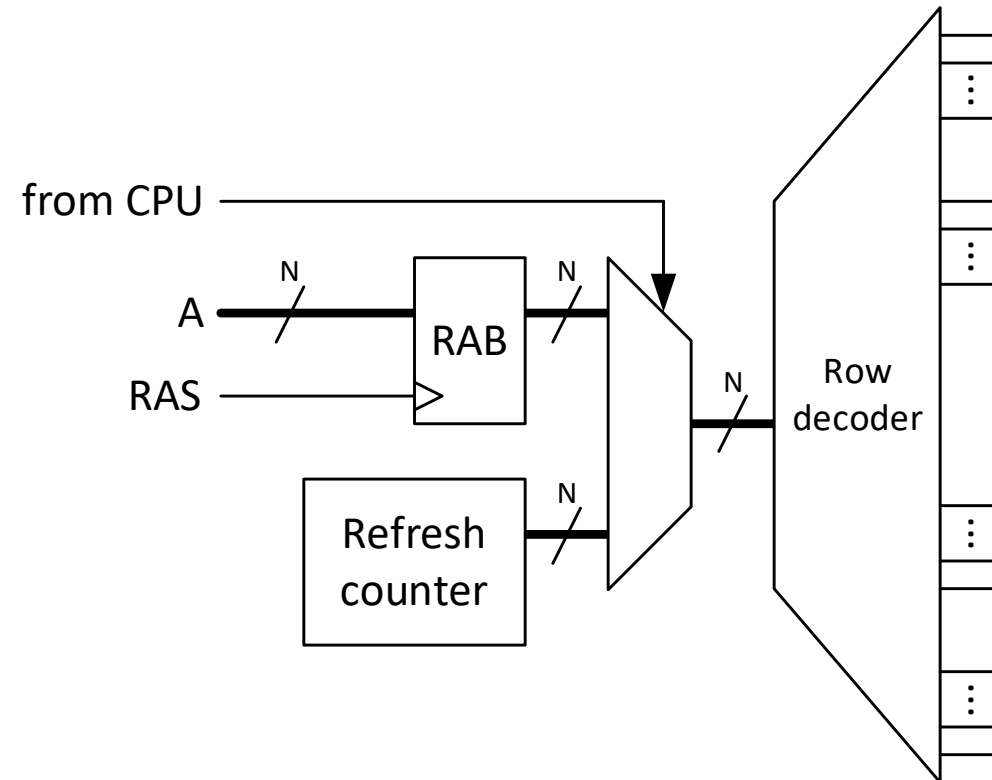- Memory bit stored inside the cells lasts at most 10 – 100 *ms*
 - **REFRESH** operation is required
 - DRAM “knows” **where** (which row) to perform the refresh
 - Counter
 - Processor/CPU “knows” **when** to perform the refresh
 - Timer



SDRAM

 
- Modern DRAMs are synchronous
 - Control and data operations referenced to a common clock signal
 - **SDRAM** = Synchronous **DRAM**
 - **Burst mode**
 - Initial latency followed by a flood of data



DDR

- **DDR = Double Data Rate**
 - SDRAM in which control and data operations are performed on both edges of clock signal
 - Rising edge
 - Falling edge
 - Data transfer rate is doubled!
 - From here the name
 - Standardized throughout the years

DDR

 

DDR

- Standards/generations

Generation	SDRAM	DDR	DDR2	DDR3	DDR4	DDR5
Year	1988	2000	2003	2007	2014	2021
Transfer rate (MT/s)	100 – 166	266 – 400	533 – 800	1066 – 1600	2133 – 5100	3200 – 6400
Data rate (GB/s)	0.8 – 1.3	2.1 – 2.3	4.2 – 4.6	8.5 – 14.9	17 – 25.6	38.4 – 51.2
Voltage (V_{CC})	3.3	2.5 – 2.6	1.8	1.35 – 1.5	1.2	1.1

Latest



Thank you for your attention

Luca Crocetti
(luca.crocetti@unipi.it)