





Electronics Systems (938II)

Lecture 2.6

Building Blocks of Electronic Systems – Timing constraints



Timing constraints

  - Do you remember of registers and flip-flops?
 - They are edge-triggered, i.e. the output change only on the triggering edge of the clock signal





Timing constraints

  - Do you remember of registers and flip-flops?
 - To work properly, the input signal (D), must be stable
 - A certain time interval **before** the (triggering) edge of clock
 - A certain time interval **after** the (triggering) edge of clock





Timing constraints

  - Do you remember of registers and flip-flops?
 - Otherwise, the register/flip-flop goes into a metastable state
 - I.e., the output is unpredictable
 - It oscillates for a while between 0 and 1, and then settles down to either 1 or 0





Timing constraints

  - Do you remember of registers and flip-flops?
 - Otherwise, the register/flip-flop goes into a metastable state
 - I.e., the output is unpredictable
 - It oscillates for a while between 0 and 1, and then settles down to either 1 or 0




Timing constraints

  - Do you remember of registers and flip-flops?
 - The interval time in which the input must be stable
 - **Before** the triggering-edge of clock is called **setup time**: t_S
 - **After** the triggering-edge of clock is called **hold time** : t_H




Timing constraints

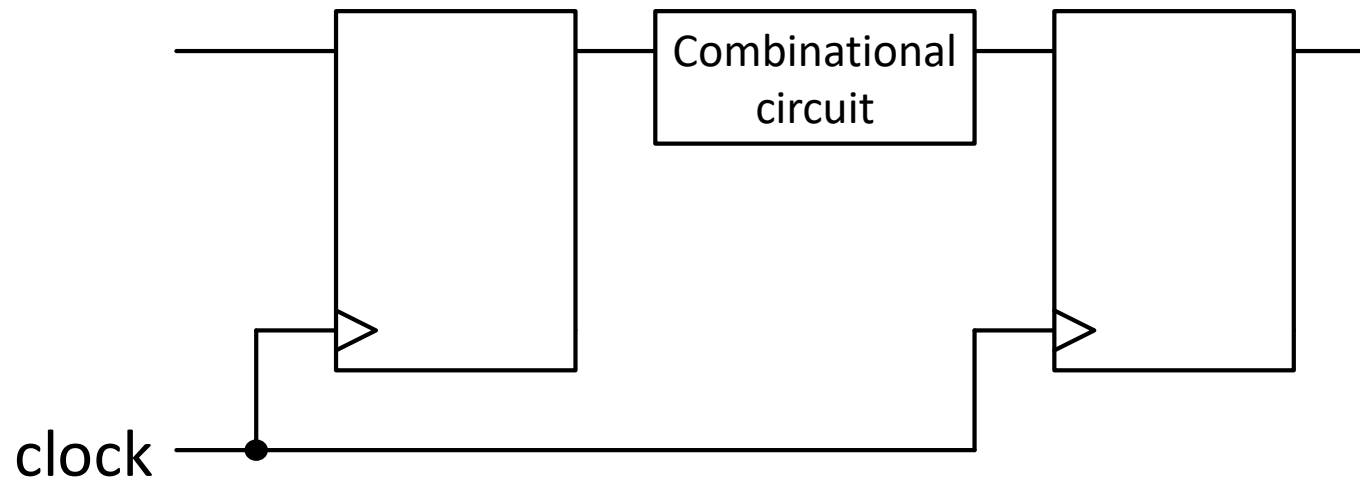- To check whether the conditions on setup and hold times are met, any digital synchronous circuit can be split in **register-to-register paths**
 - RTL representation of the circuit




Register-to-register path

- An example
 - How many paths?

 


Register-to-register path

- An example
 - How many paths?
 - 4!

 


Register-to-register path

 - An example
 - How many paths?
 - 4!
 - 1




Register-to-register path

 - An example
 - How many paths?
 - 4!
 - 2




Register-to-register path

 - An example
 - How many paths?
 - 4!
 - 3




Register-to-register path

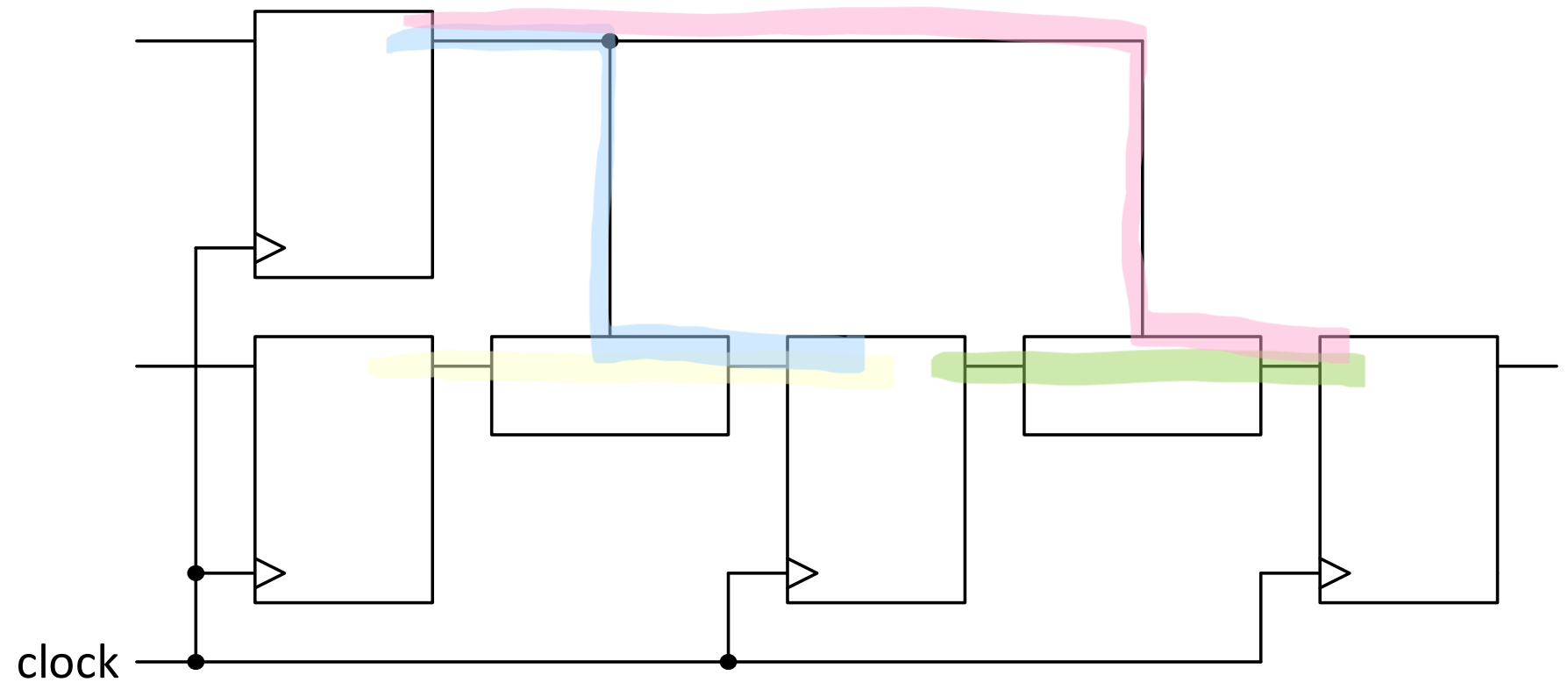- An example
 - How many paths?
 - 4!
 - 4




Register-to-Register path

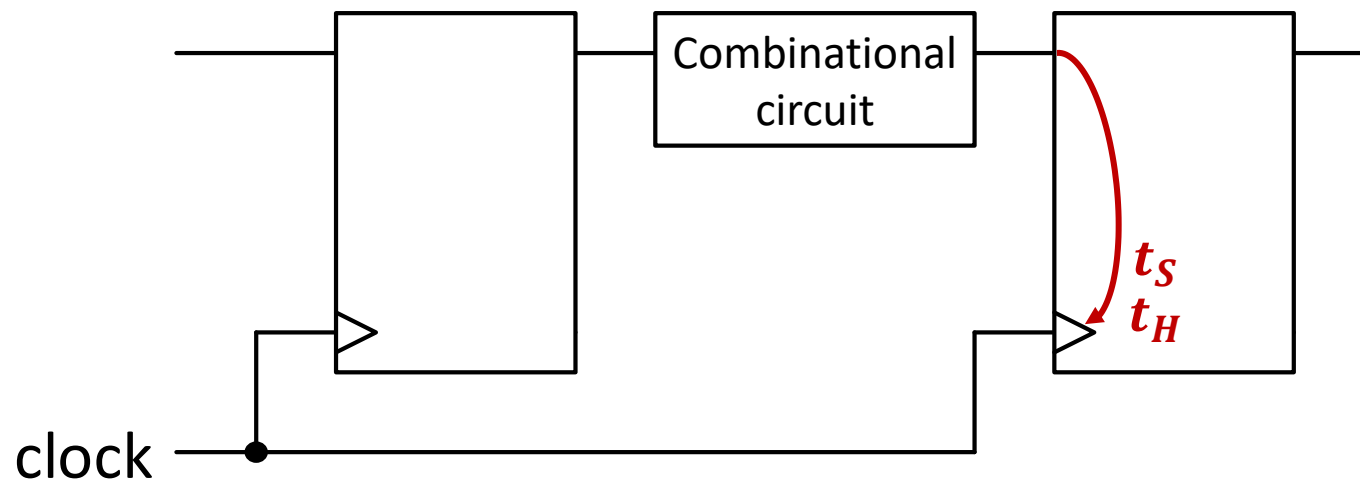- Setup and hold times refer to the path between input data and clock




Register-to-Register path

 - However, for this analysis, also other time intervals must also be considered




Register-to-Register path

 - However, for this analysis, also other time intervals must also be considered
 - t_{pd} = **propagation delay** of **combinational** circuit between the registers




Register-to-Register path

 - However, for this analysis, also other time intervals must also be considered
 - t_{co} = **clock-to-output time**, i.e. the time required to settle a valid output on an output pin after a clock transition




Register-to-Register path

 - In addition
 - The source register is called the **launch register**, and the corresponding clock signal is called the **launch clock**




Register-to-Register path

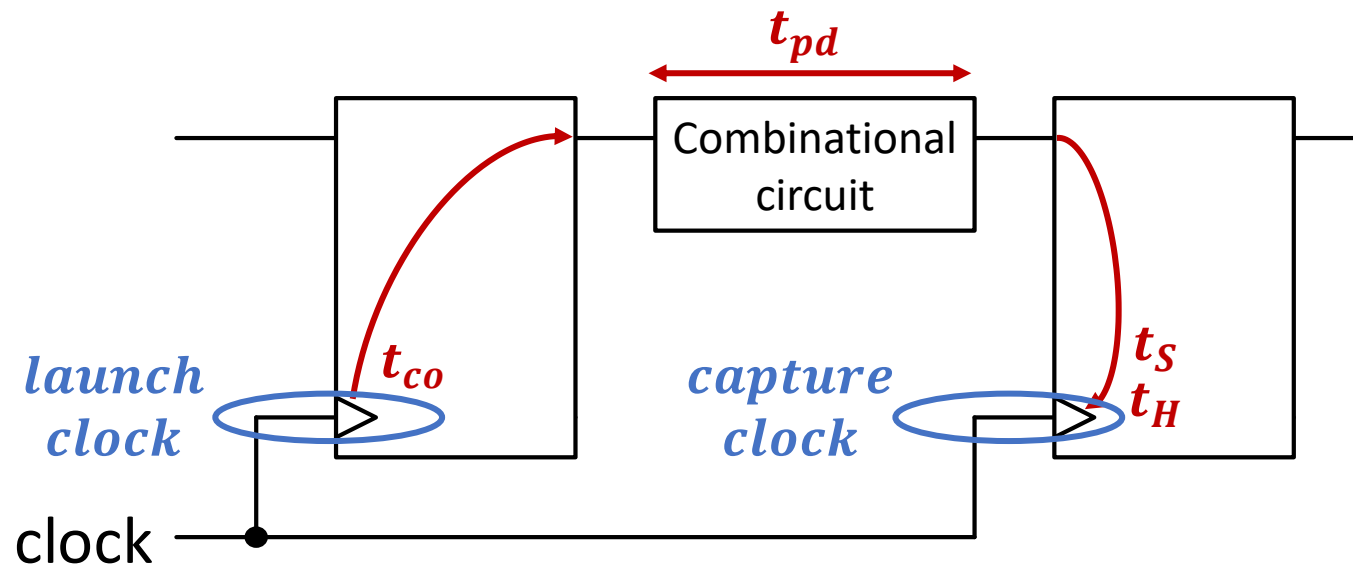- In addition
 - The destination register is called the **capture register**, and the corresponding clock signal is called the **capture clock**




Register-to-Register path

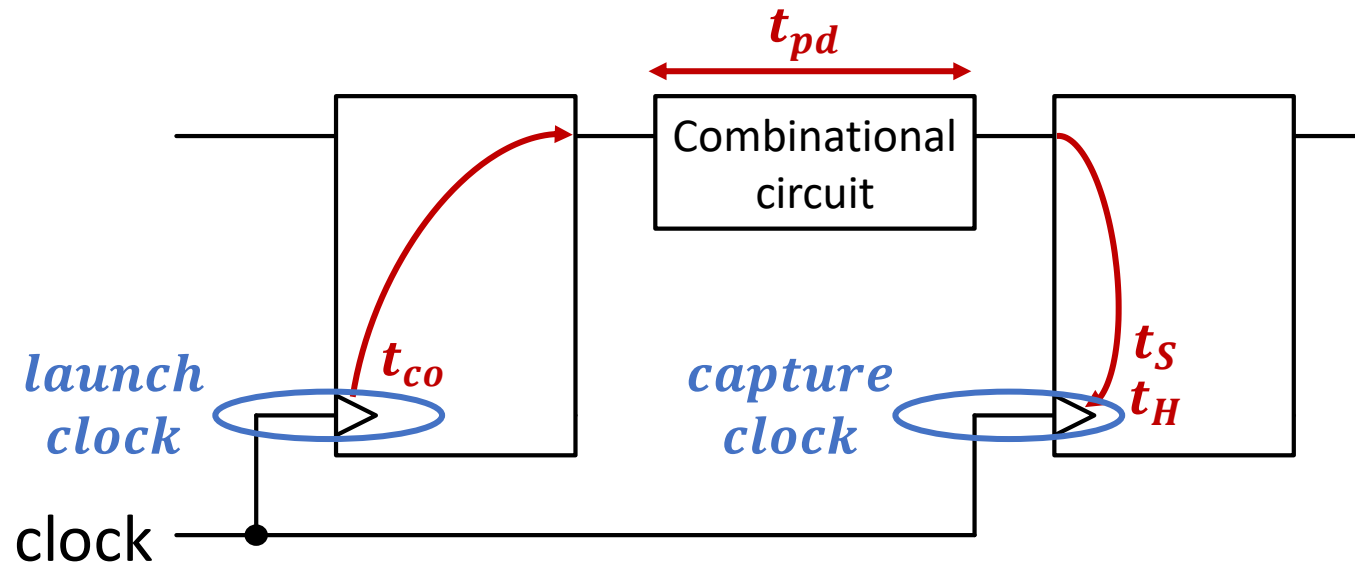- Ideally, the launch and capture clocks are the same signal with a **period** T_{clk} , but let's consider them as two distinct signals
 - It depends on the circuit manufacturing process
 - Trust me for a while




Timing constraints – Setup time

 
- Let's start by determining the timing constraint on the setup time
 - Let's define the points
 - **A** = the output pin of the launch register
 - **B** = the input pin of the capture register



Timing constraints – Setup time

 


Timing constraints – Setup time

 


If $t_2 > t_3$, the change of input to the capture register (B) falls in the setup time, so ...

Timing constraints – Setup time

 


Timing constraints – Setup time

 - $t_2 = t_1 + t_{co} + t_{pd}$
- $t_3 = t_4 - t_s$




Timing constraints – Setup time

 


Timing constraints – Setup time

- $t_4 = t_1 + T_{clk}$

 

Timing constraints – Setup time

 


$$t_1 + t_{co} + t_{pd} \leq t_1 + T_{clk} - t_s$$


Timing constraints – Setup time

$$t_1 + t_{co} + t_{pd} \leq t_1 + T_{clk} - t_S$$


Timing constraints – Setup time

$$\cancel{t_1} + t_{co} + t_{pd} \leq \cancel{t_1} + T_{clk} - t_s$$


Timing constraints – Setup time

$$\cancel{t_1} + t_{co} + t_{pd} \leq \cancel{t_1} + T_{clk} - t_s \quad \Rightarrow \quad t_s + t_{co} + t_{pd} \leq T_{clk}$$


Timing constraints – Setup time

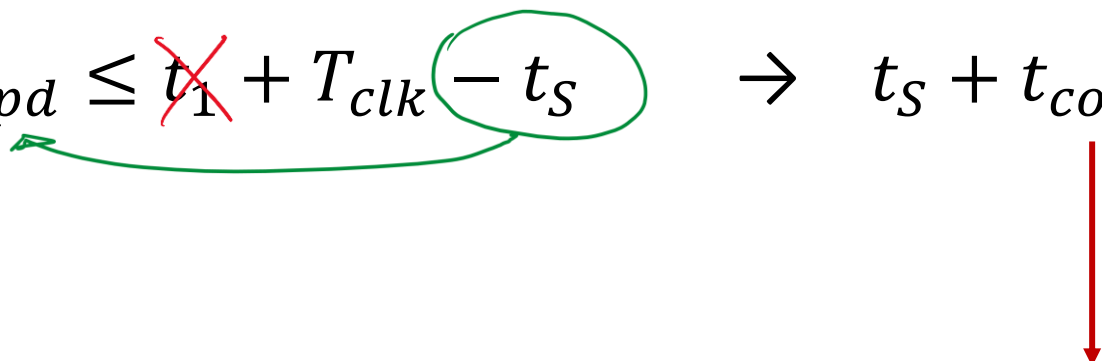
$$\cancel{t_1} + t_{co} + t_{pd} \leq \cancel{t_1} + T_{clk} - t_s \quad \Rightarrow \quad t_s + t_{co} + t_{pd} \leq T_{clk}$$


$$T_{clk} \geq t_s + t_{co} + t_{pd}$$

Timing constraints – Setup time

- To be honest, the propagation delay can be characterized by a minimum and maximum value

- $t_{pd_{max}}$
- $t_{pd_{min}}$

 

Timing constraints – Setup time

- $T_{clk} \geq t_S + t_{co} + t_{pd}$

- $t_{pd} ? = ? \begin{cases} t_{pd_{min}} \\ t_{pd_{max}} \end{cases}$

Timing constraints – Setup time

- $T_{clk} \geq t_S + t_{co} + t_{pd}$

- $t_{pd} ? = ? \begin{cases} t_{pd_{min}} \\ t_{pd_{max}} \end{cases} \rightarrow \text{Worst case!}$

Timing constraints – Setup time

- $T_{clk} \geq t_S + t_{co} + t_{pd}$
- $t_{pd} ? = ? \begin{cases} t_{pd_{min}} \\ t_{pd_{max}} \end{cases} \rightarrow \text{Worst case!}$
- Why the worst case ($t_{pd_{max}}$) ?

Timing constraints – Setup time

- $T_{clk} \geq t_S + t_{co} + t_{pd}$

- $t_{pd} ? = ? \begin{cases} t_{pd_{min}} \\ t_{pd_{max}} \end{cases} \rightarrow \text{Worst case!}$

- Why the worst case ($t_{pd_{max}}$) ?
- Because if the circuit works in the worst conditions, for sure it works also in the other conditions: typical, best

Timing constraints – Setup time

- Summarizing, the timing constraint on the setup time (t_S) is

$$T_{clk} \geq t_S + t_{co} + t_{pd_{max}}$$

Timing constraints – Setup time and clock frequency

- Summarizing, the timing constraint on the setup time (t_S) is

$$T_{clk} \geq t_S + t_{co} + t_{pd_{max}}$$

- The clock frequency is $f_{clk} = \frac{1}{T_{clk}}$, so the clock frequency must satisfy

$$f_{clk} \leq \frac{1}{t_S + t_{co} + t_{pd_{max}}}$$

Timing constraints – Setup time and clock frequency


- $f_{clk} \leq \frac{1}{t_S + t_{co} + t_{pd_{max}}}$

- Therefore, the maximum frequency is:


$$f_{clk_{max}} = \frac{1}{t_S + t_{co} + t_{pd_{max}}}$$

Timing constraints – Hold time

 
- Now let's move to the timing constraint on the hold time



Timing constraints – Hold time

 


Timing constraints – Hold time

 


If $t_7 < t_6$, the change of input to the capture register (B) falls in the hold time, so ...

Timing constraints – Hold time

 


Timing constraints – Hold time

 - $t_7 = t_5 + t_{co} + t_{pd}$
- $t_6 = t_5 + t_H$



Timing constraints – Hold time

 

Timing constraints – Hold time

$$t_5 + t_{co} + t_{pd} \geq t_5 + t_H$$

Timing constraints – Hold time

$$\cancel{t_5} + t_{co} + t_{pd} \geq \cancel{t_5} + t_H$$

Timing constraints – Hold time

$$\cancel{t_5} + t_{co} + t_{pd} \geq \cancel{t_5} + t_H \quad \rightarrow \quad t_{co} + t_{pd} \geq t_H$$

Timing constraints – Hold time

$$\cancel{t_5} + t_{co} + t_{pd} \geq \cancel{t_5} + t_H \quad \rightarrow \quad t_{co} + t_{pd} \geq t_H$$



$$t_H \leq t_{co} + t_{pd}$$

Timing constraints – Hold time

- $t_H \leq t_{co} + t_{pd}$
 - $t_{pd} ? = ? \begin{cases} t_{pd_{min}} \\ t_{pd_{max}} \end{cases}$

Timing constraints – Hold time

- $t_H \leq t_{co} + t_{pd}$
- $t_{pd} ? = ? \begin{cases} t_{pd_{min}} \\ t_{pd_{max}} \end{cases} \rightarrow \text{Worst case!}$
- Again, worst case for the same reasons

Timing constraints – Hold time

- Summarizing, the timing constraint on the hold time (t_H) is

$$t_H \leq t_{co} + t_{pd_{min}}$$

Timing constraints

- Summary

- Setup $\rightarrow T_{clk} \geq t_S + t_{co} + t_{pd_{max}} \rightarrow \left(f_{clk} \leq \frac{1}{t_S + t_{co} + t_{pd_{max}}} \right)$

- Hold $\rightarrow t_H \leq t_{co} + t_{pd_{min}}$

Timing constraints

- Summary

- Setup $\rightarrow T_{clk} \geq t_S + t_{co} + t_{pd_{max}} \rightarrow \left(f_{clk} \leq \frac{1}{t_S + t_{co} + t_{pd_{max}}} \right)$

- Hold $\rightarrow t_H \leq t_{co} + t_{pd_{min}}$

- Is it ALL the truth?

Timing constraints

- Summary

- Setup $\rightarrow T_{clk} \geq t_S + t_{co} + t_{pd_{max}} \rightarrow \left(f_{clk} \leq \frac{1}{t_S + t_{co} + t_{pd_{max}}} \right)$

- Hold $\rightarrow t_H \leq t_{co} + t_{pd_{min}}$

- Is it ALL the truth? No!



- Some aspects are still missing

Timing constraints

- Modern digital systems count a lot of transistors
 - We saw about VLSI: transistor count $\geq 10^6$
 - In some case up to 10^{10}
 - Part of these transistors are used for registers/flip-flops
 - A single clock signal must reach (physically) many registers
 - Ideally at the same time
 - However, this is not physically possible (because of the high density of registers)

Timing constraints

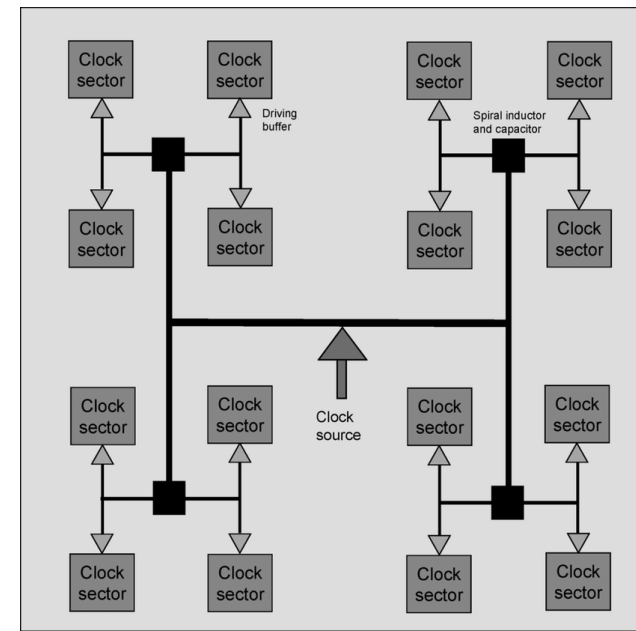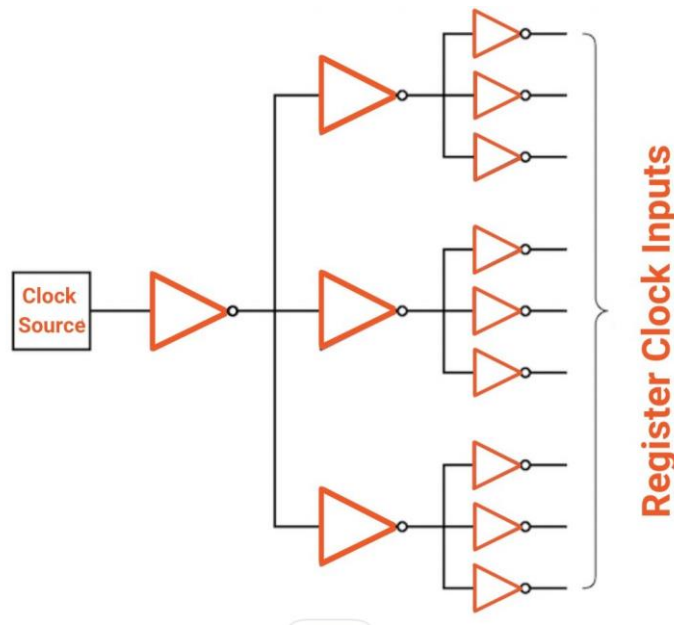- The clock distribution is a very delicate aspect of the chip manufacturing process
 - It constitutes a specific and dedicated step of the manufacturing process: CTS (Clock Tree Synthesis)
 - They exist techniques to optimize the distribution of clock and equalize it as much as possible




Timing constraints

- Anyway, is not physically possible to make the distance between the clock source and the clock port of registers equal for all the registers
- And even if so, other (physical, and unpredictable) factors may cause delays on the clock between different registers
 - Temperature variations
 - Material imperfections
 - ...


Timing constraints

 - Therefore, the delay model should include also the delay between the launch clock and the capture clock
 - It is called **skew** and typically indicated with δ




Timing constraints

 - This slightly changes the previous constraints we determined



Timing constraints

 - In addition, also the wires delay (t_{w_i}) should be considered




Timing constraints

- And they exist corner cases that we did not consider


Timing constraints

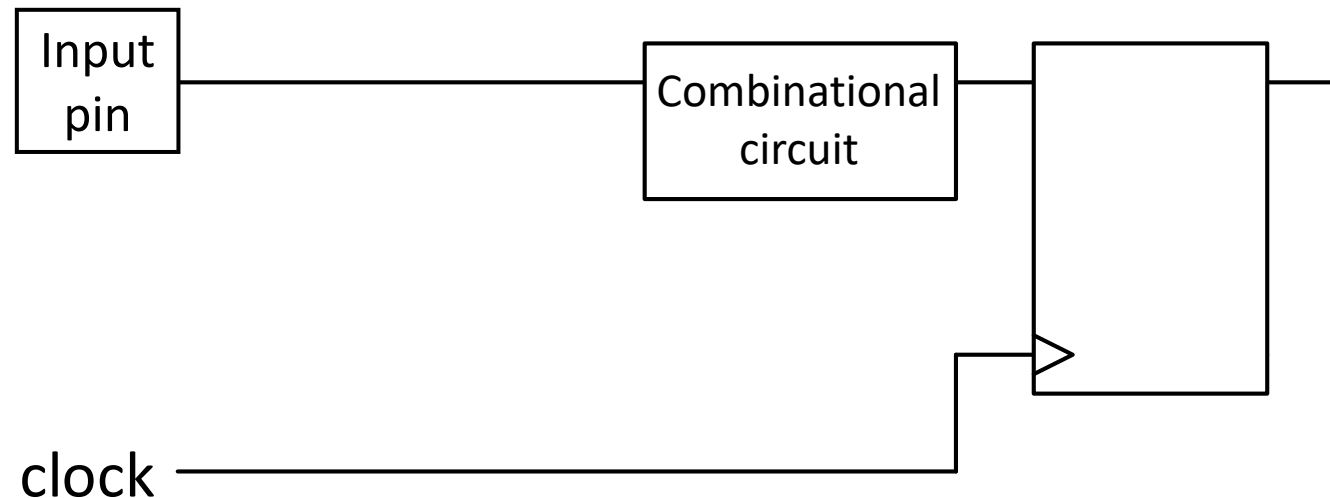- And they exist corner cases that we did not consider
 - Input paths
 - Launch register misses





Timing constraints

 - And they exist corner cases that we did not consider
 - Output paths
 - Capture register misses




Timing constraints

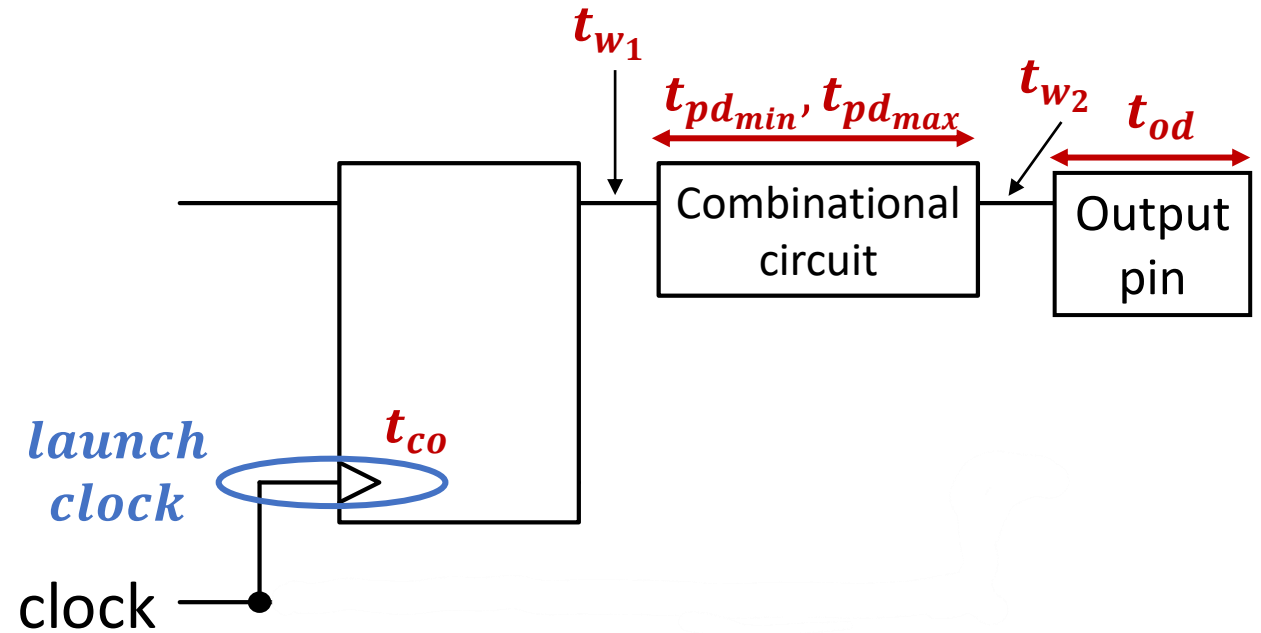 - Input and output paths would require a more accurate delay model
 - t_{id} = input delay (of the input pin)
 - t_{od} = output delay (of the output pin)




Timing constraints

 - And they exist corner cases that we did not consider
 - Others
 - Combinational logic misses



Both registers miss (combinational path)

 

Timing constraints

- We are going to analyze the more accurate delay models
- However, remember that
 - The timing analysis to check the setup and hold constraints are met is an essential part of the design process of a circuit
 - It is automated and called **STA** = **S**tatic **T**iming **A**alysis
 - It can be performed multiple times/at different level, since any step of the design process can add information about timing
 - Gate-level → information about gate delays
 - Transistor-level → information about delays of wires, pins, ...

Timing constraints

- Also remember that
 - Setup violations
 - Can be fixed during design phase
 - Frequency lowering, insertion of pipeline(s) to reduce the path delay, ...
 - Can be fixed after the fabrication of the chip
 - Frequency lowering
 - Hold violations
 - Can be fixed during design phase
 - Inserting delay chains (e.g., cascade of NOT gates or buffers)
 - Cannot be fixed after the fabrication of the chip!!!



Thank you for your attention

Luca Crocetti
(luca.crocetti@unipi.it)