



# Electronics Systems (938II)

## Lecture 3.2


### Semiconductor Memories – ROM and PROM

# ROM

- **ROM = Read-Only Memory**
  - However, this gives information only on the supported operation(s)
    - I.e., read-only (not write)
  - It does not give information on the access mode (random or sequential)
    - Typically, this kind of memories supports random access
      - I.e., any arbitrary address can be accessed immediately
    - So, it is also a RAM
      - Please, do not confuse with the computer memory typically called RAM, which is a RAM (from the perspective of access mode), but it is also a RWM (Read-Write Memory)
 
# ROM – Architecture

- Brief reminder of the structure of semiconductor memories
  - $WL_i$  = Word Line
  - $BL_j$  = Bit Line




# ROM – Architecture

- Brief reminder of the structure of semiconductor memories


- $WL_i$  = Word Line
- $BL_j$  = Bit Line

- In case of ROM, the memory cell can be

- 1 n-MOS transistor

 

- Empty

 


# ROM – Architecture

- Memory cell – n-MOS transistor

- $WL_i$  = Word Line
- $BL_j$  = Bit Line


- n-MOS

- D = Drain
- G = Gate
- S = Source

 
 
# ROM – Architecture

- Memory cell – n-MOS transistor
  - $WL_i$  = Word Line
  - $BL_j$  = Bit Line
- n-MOS
  - D = Drain
  - G = Gate
  - S = Source
- To complete the architecture ...



# ROM – Architecture

- Memory cell – n-MOS transistor


- $WL_i$  = Word Line
- $BL_j$  = Bit Line

- n-MOS

- D = Drain
- G = Gate
- S = Source


- R = Resistor

 - Pull-up resistor: connect  $BL_j$  to  $V_{CC}$  = high logic level (1)


 
# ROM – Architecture


- Memory cell – n-MOS transistor
  - Principle of operation




 
# ROM – Architecture

- Memory cell – n-MOS transistor
  - Principle of operation
    - $WL_i = 0$ 
      - n-MOS = OFF (open circuit)
      - $BL_j = 1$  (because of pull-up resistor)




# ROM – Architecture

- Memory cell – n-MOS transistor


- Principle of operation

 - $WL_i = 0$ 
  - n-MOS = OFF (open circuit)
  - $BL_j$  = 1 (because of pull-up resistor)
- $WL_i = 1$ 
  - n-MOS = ON (short circuit)
  - $BL_j$  = 0 (ground connection through the n-MOS)


 
# ROM – Architecture

- Memory cell – Empty
  - Principle of operation
    - $WL_i = 0$ 
      - $BL_j = 1$  (because of pull-up resistor)
    - $WL_i = 1$ 
      - $BL_j = 1$  (because of pull-up resistor)



# ROM – Architecture

- Memory cell – Summary
  - Principle of operation


Memory cell	Word Line ( $WL_i$ )	Bit Line ( $BL_j$ )
With n-MOS	0 (disabled)	1
	1 (enabled)	0
Empty	0 (disabled)	1
	1 (enabled)	1

# ROM – Architecture

- Integrating the row and column decoders to complete the architecture
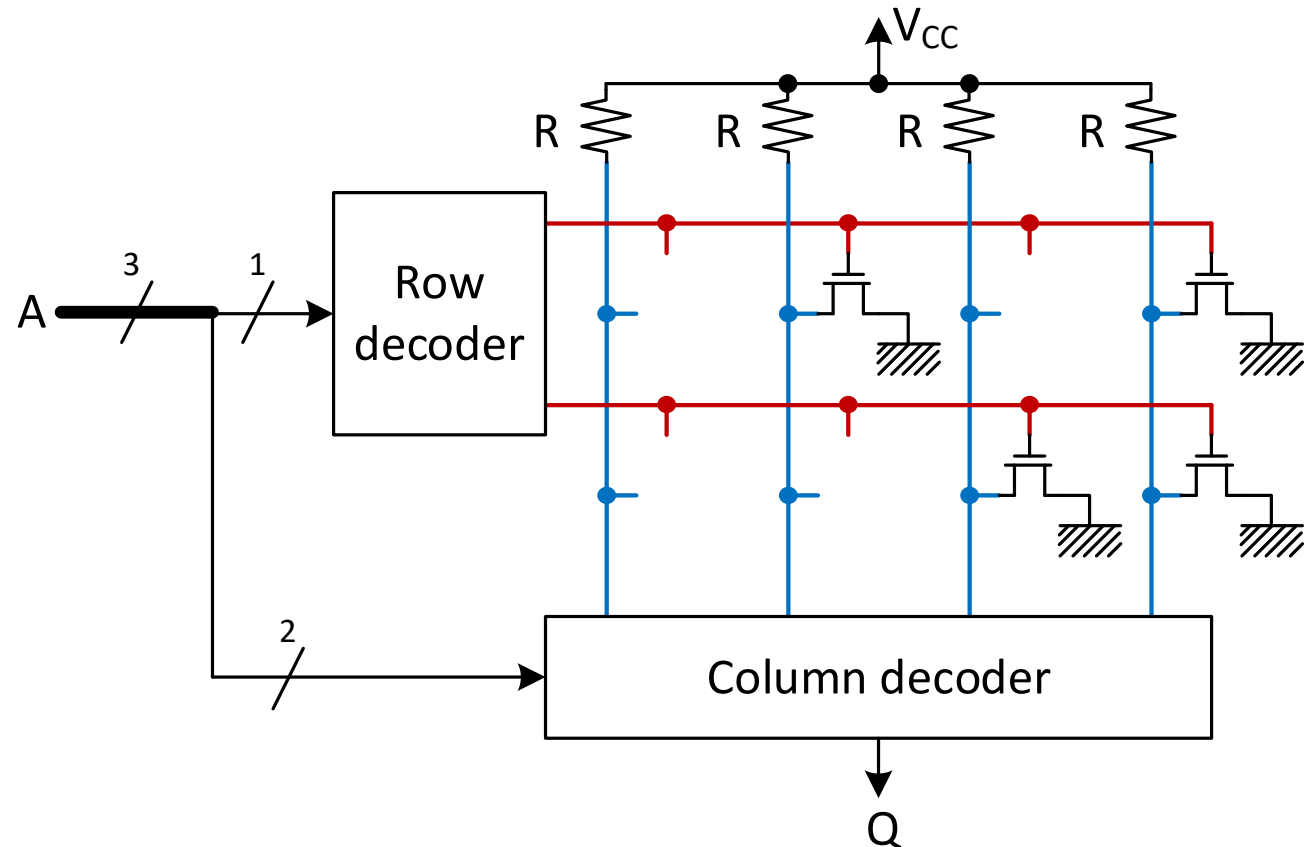
# ROM – Architecture

- Integrating the row and column decoders to complete the architecture
  - Example on a 2x4 ROM
    - A = Address (3-bit)
    - Q = single-bit output




# ROM – Architecture

- Integrating the row and column decoders to complete the architecture

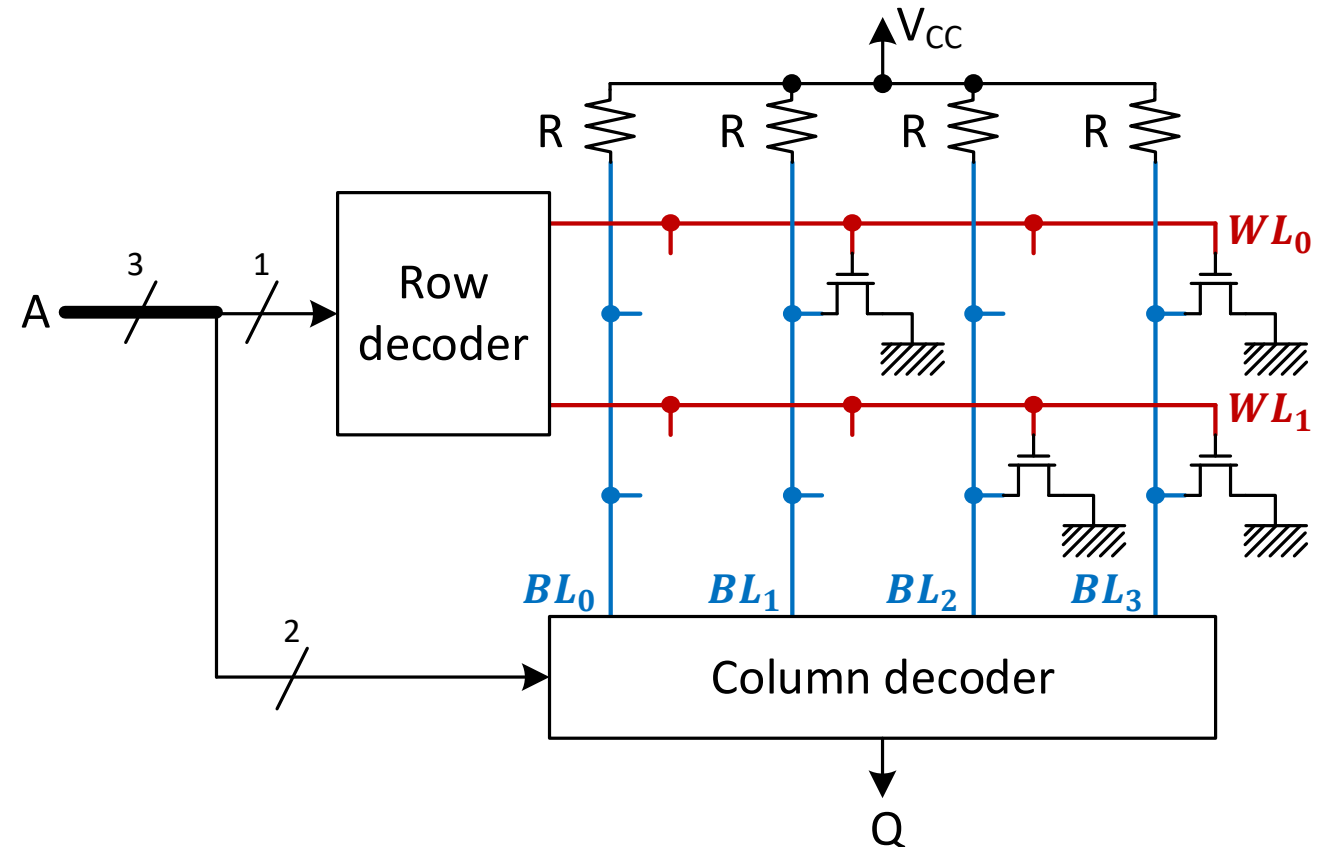- Example on a 2x4 ROM

- A = Address (3-bit)
  - Q = single-bit output
- Assume cell (x,y)
  - $WL_x$
  - $BL_y$



# ROM – Architecture

- Integrating the row and column decoders to complete the architecture


- Example on a 2x4 ROM

- A = Address (3-bit)
- Q = single-bit output

- Assume **cell (x,y)**

- $WL_x$
- $BL_y$

- Assume to read **cell (1,1)**

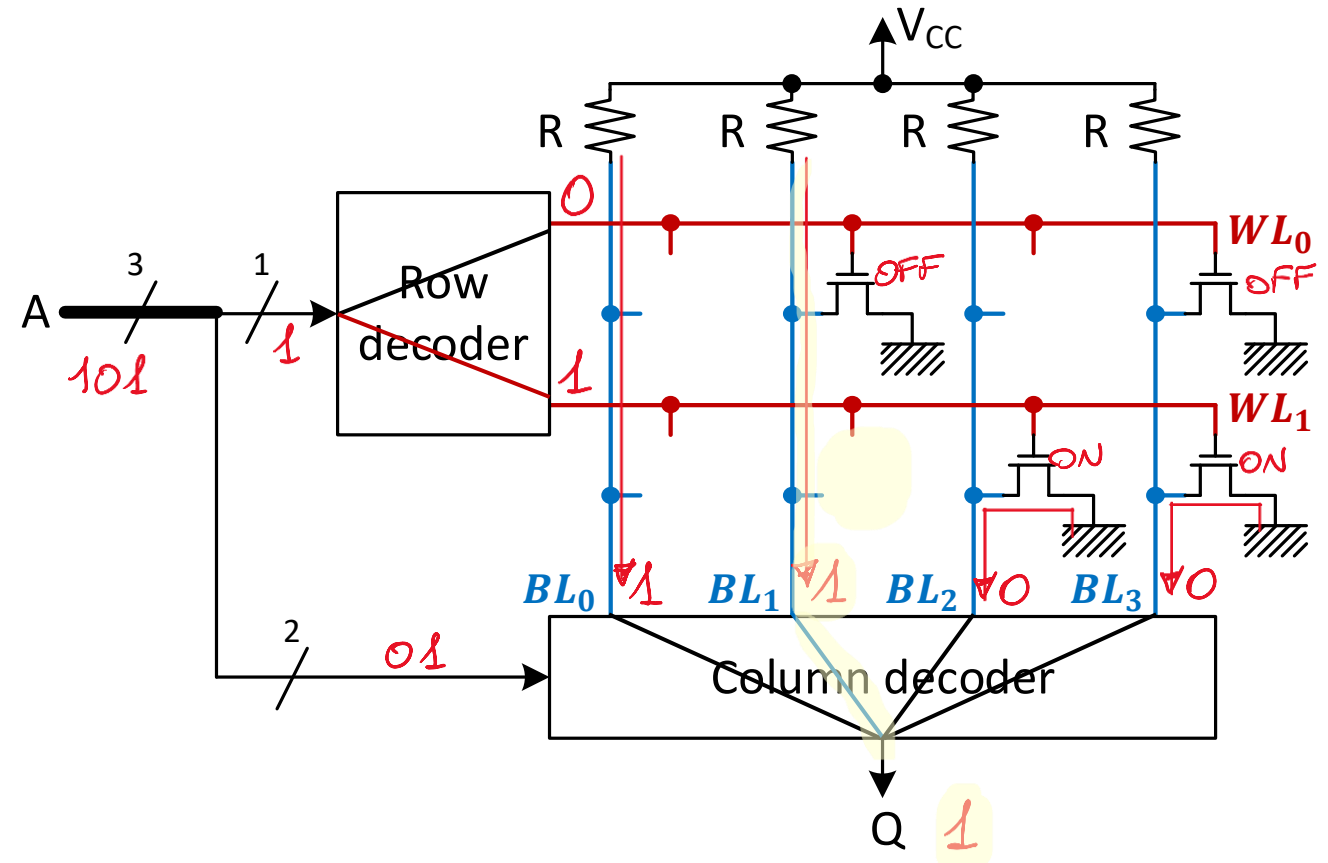



# ROM – Architecture

- Integrating the row and column decoders to complete the architecture


- Example on a 2x4 ROM

- A = Address (3-bit)
- Q = single-bit output

- Assume **cell (x,y)**

- $WL_x$
- $BL_y$

- Assume to read **cell (0,1)**

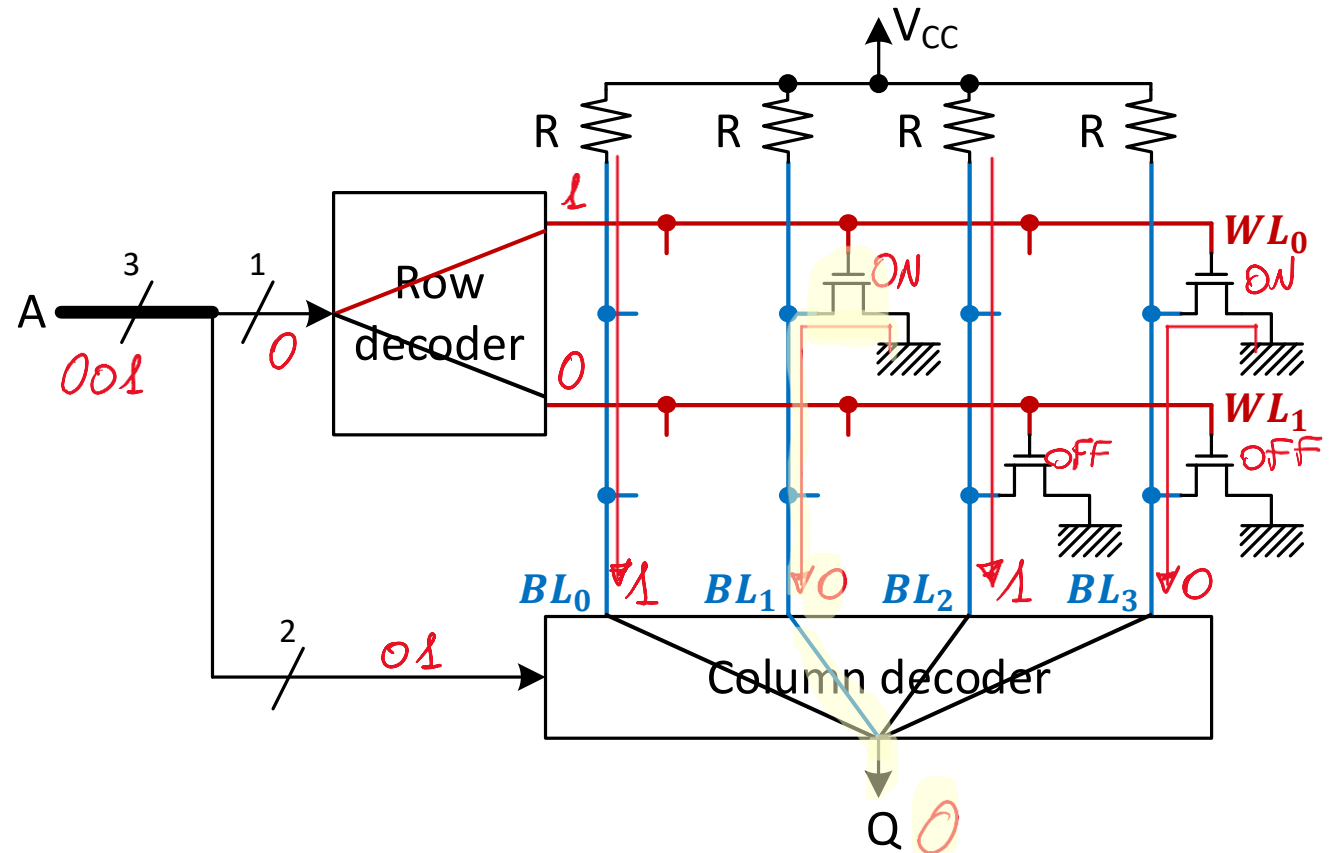

# ROM – Architecture

- Integrating the row and column decoders to complete the architecture


- Example on a 2x4 ROM

- A = Address (3-bit)
- Q = single-bit output

- Assume **cell (x,y)**

- $WL_x$
- $BL_y$

- Assume to read **cell (1,3)**

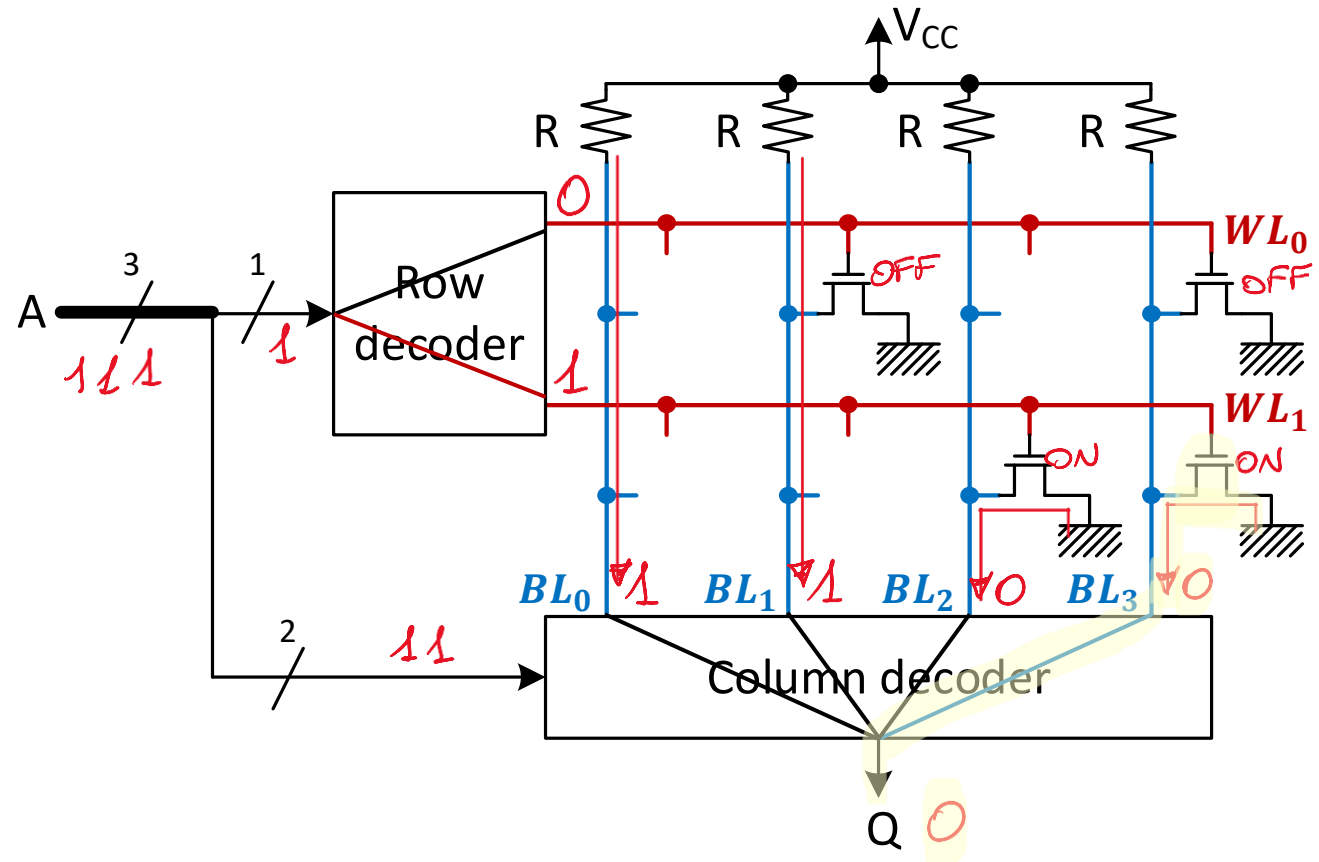

# ROM – Architecture

- Integrating the row and column decoders to complete the architecture


- Example on a 2x4 ROM

- A = Address (3-bit)
- Q = single-bit output

- Assume **cell (x,y)**

- $WL_x$
- $BL_y$

- Assume to read **cell (0,3)**

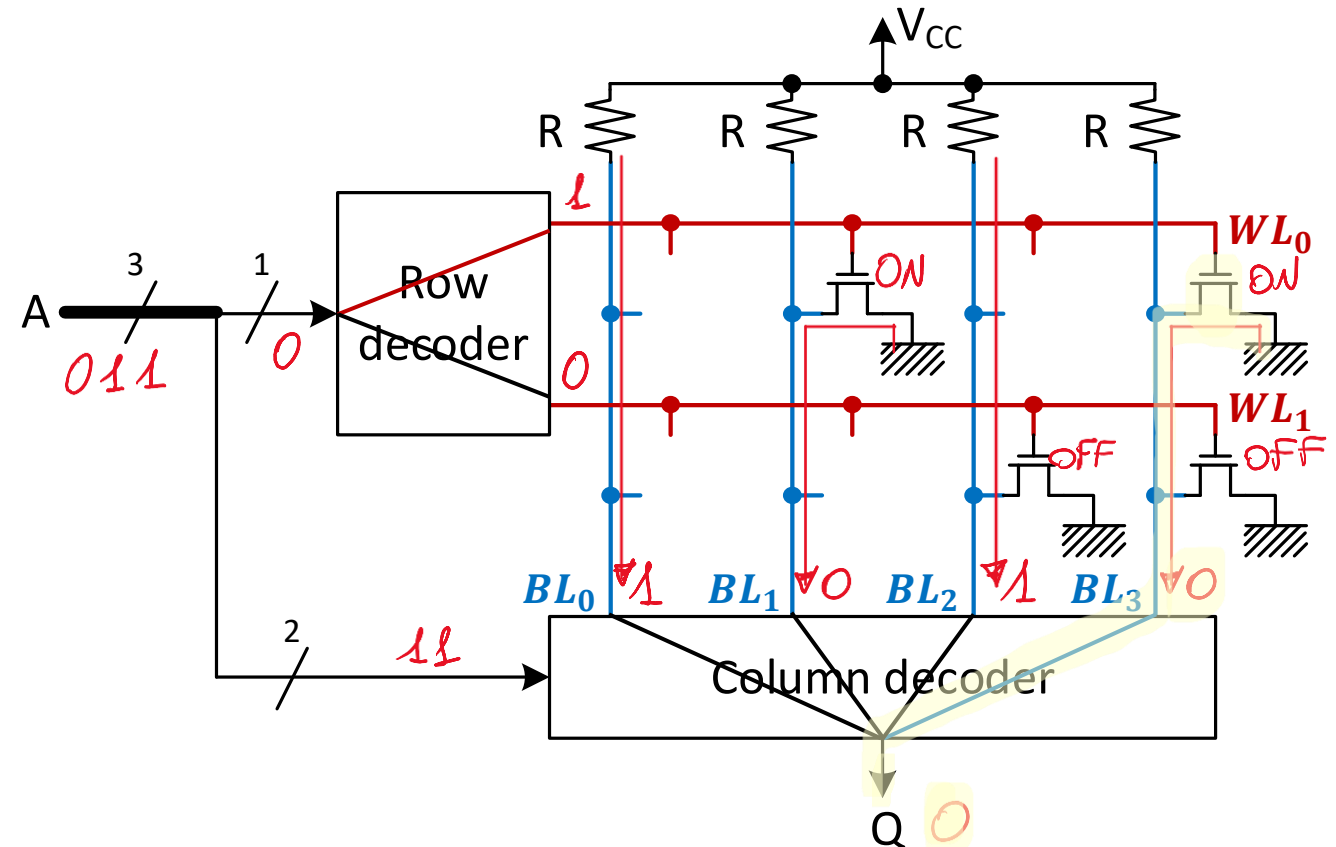


## ROM – Architecture

- So, when reading (i.e. enabling corresponding word line and bit line) a memory cell
  - With (n-MOS) transistor  $\rightarrow$  Output = 0
  - Empty (without transistor)  $\rightarrow$  Output = 1
- However, also solutions with active-low decoding logic (for column decoder) exist

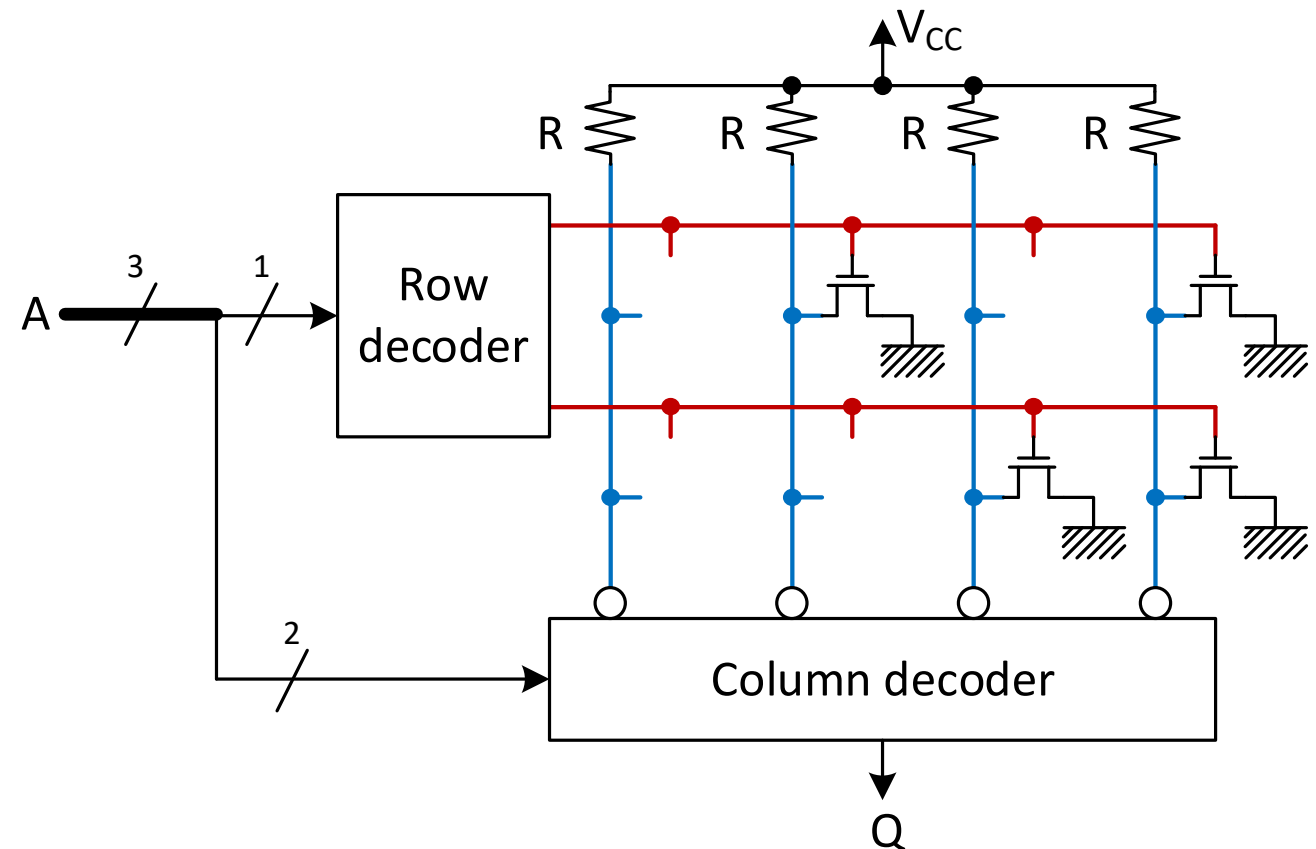
# ROM – Architecture

- Active-low decoding logic (column decoder)
  - Example on a 2x4 ROM


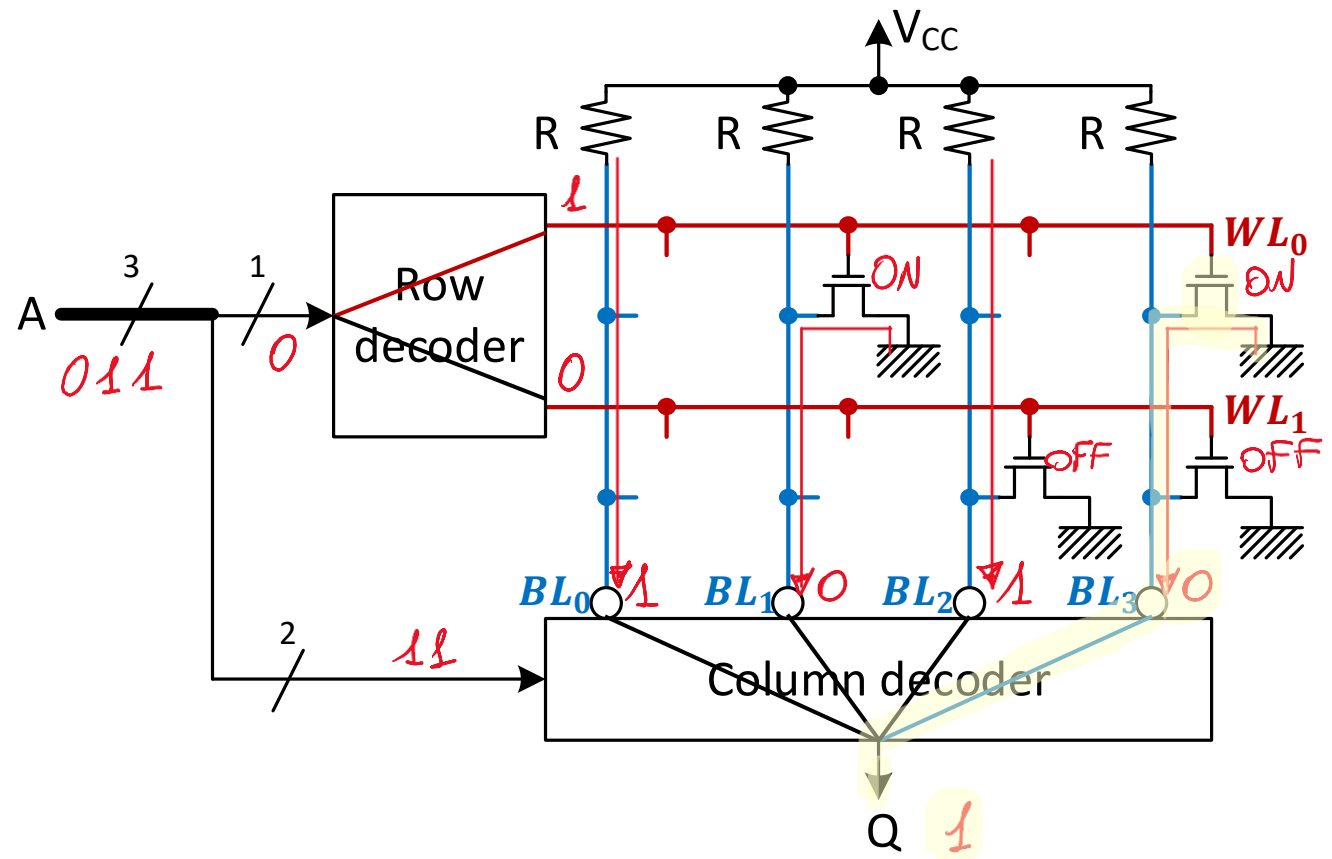
# ROM – Architecture

- Active-low decoding logic (column decoder)
  - Example on a 2x4 ROM
    - Assume to read **cell (0,3)**



## ROM – Architecture

- When reading a memory cell when column decoder is active-low
  - With (n-MOS) transistor → Output = 1
  - Empty (without transistor) → Output = 0
- The opposite of the previous case

# ROM – Architecture

- Content of memory cells
  - The output (bit) corresponds to the content of memory cells, since that is what is obtained by reading that cell

Memory cell	Bit Line ( $BL_j$ )	Output (bit) = Content	
		Active-high decoding logic	Active-low decoding logic
With n-MOS	0	0	1
Empty	1	1	0



# ROM – Remarks and applications

- The one shown is called also **mask-ROM**
  - Remember about the photolithographic masks employed in the semiconductor manufacturing process
  - Each memory content corresponds to a different layout (of transistors), or, in other words, to a different integrated circuit
  - Thus, to a different mask to realize that layout (or circuit)

## ROM – Remarks and applications

- Photolithographic masks have high costs
  - Only for applications that require high volumes of ROM
- Memory content cannot be modified
  - The modification of just one bit (due to updates or bugs) means wasting the entire chip (and all other chips with the same content)
  - Only for solid applications for which you are largely sure about the content of the memory

# PROM

- In the course of technological progress, mask-ROM has evolved into **Programmable ROM (PROM)**
  - Still a ROM, Read-Only Memory
  - But whose content is defined after the manufacture (of the integrated circuit)
    - Not during the manufacture like the mask-ROM
  - This allowed for a reduction in production costs because ...
    - For mask-ROMs: different memory content → different integrated circuit → different production line (masks, ...)
    - For PROM: always the same integrated circuit → the same production line

# PROM


- So, after production the PROM must be “written” to define its content
  - This operation is called Programming
    - From here the name
  - Just one time
    - OTP = One Time Programmable

# PROM

- So, after production the PROM must be “written” to define its content
  - This operation is called Programming
    - From here the name
  - Just one time
    - OTP = One Time Programmable
- For this purpose, each memory cell contains **a transistor + a fuse**
  - The **fuse** is an electronic component that ...
    - ... by default, is a connection (a short circuit)
    - ... when subjected to a very strong current, it breaks down, breaking the connection (it becomes an open circuit)


# PROM – Architecture

- Memory cell

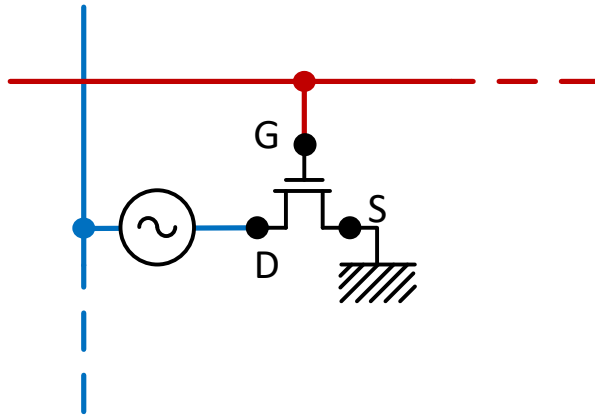


# PROM – Architecture

- Memory cell
  - Transistor (n-MOS)

 
 
# PROM – Architecture



- Memory cell
  - Transistor (n-MOS)
  - Fuse





  
# PROM – Architecture

- Memory cell
  - Transistor (n-MOS)
  - Fuse


 
# PROM – Architecture

- Memory cell
  - Transistor (n-MOS)
  - Fuse




## PROM – Principle of operation

- Thus, programming means selecting which fuses to break (by injecting a high current)
  - Programmed fuse            = broken fuse            = open circuit
  - Unprogrammed fuse        = default-state fuse      = short circuit
 
## PROM – Principle of operation

- For this purpose, high voltage pulses ( $V_{pp} = 10/30$  V) must be applied to
  - Gate terminal of n-MOS = Word Line
  - Drain terminal of n-MOS = Bit Line
  - n-MOS is in “high conduction” region = very high current




## PROM – Principle of operation

- By selecting (only) the corresponding Word Line and Bit Line, each memory cell can be programmed (or not) without the risk of accidentally programming cells that should do not
  - A dedicated interface is required
- After programming, the PROM works exactly like the mask-ROM
  - Not programmed cell = cell with transistor → 0 on BL → 0/1 on output (Q)
  - Programmed cell  $\cong$  empty cell → 1 on BL → 1/0 on output (Q)


# PROM – Principle of operation

- Example
  - Before programming

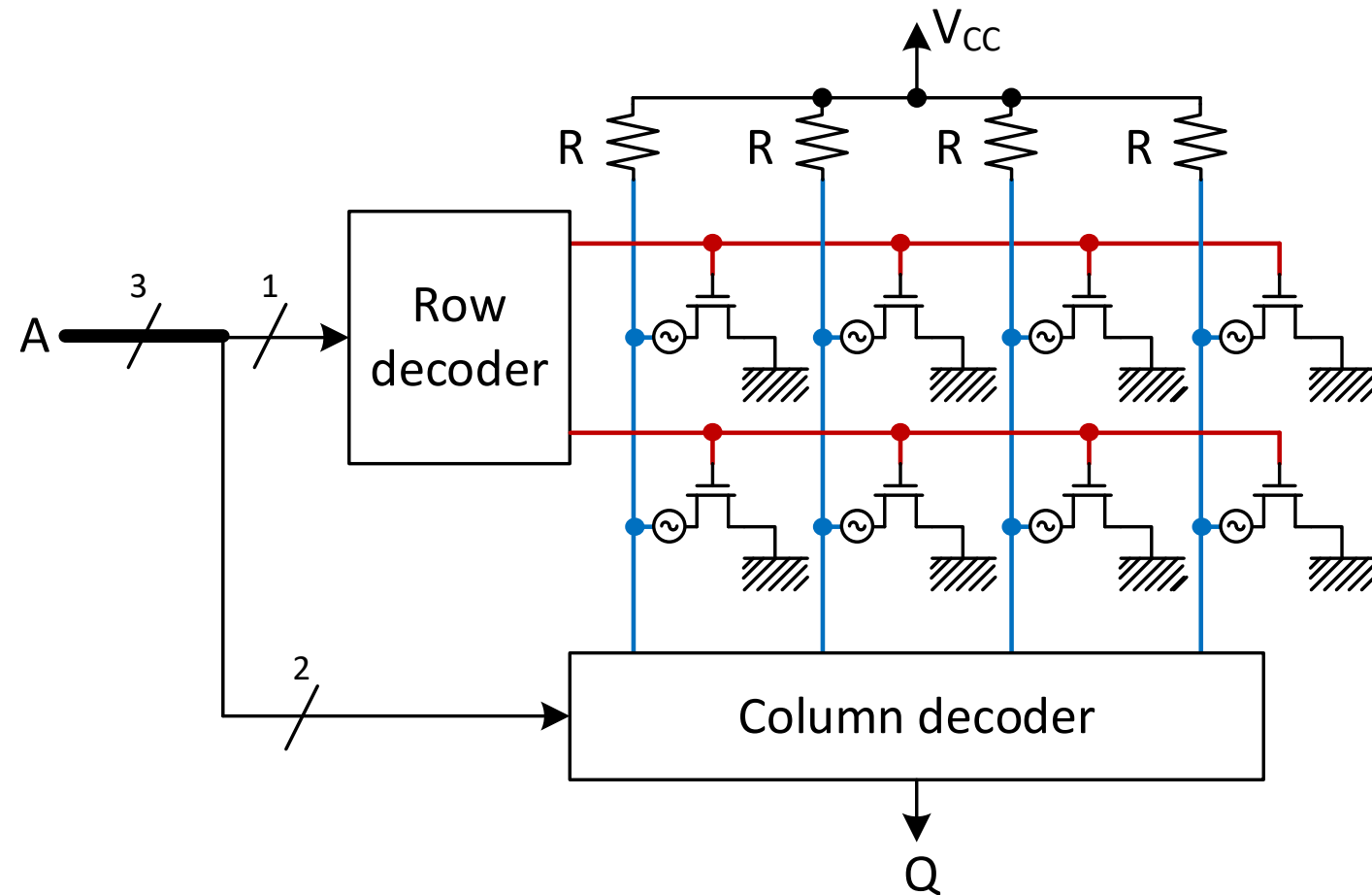


# PROM – Principle of operation

- Example
  - After programming

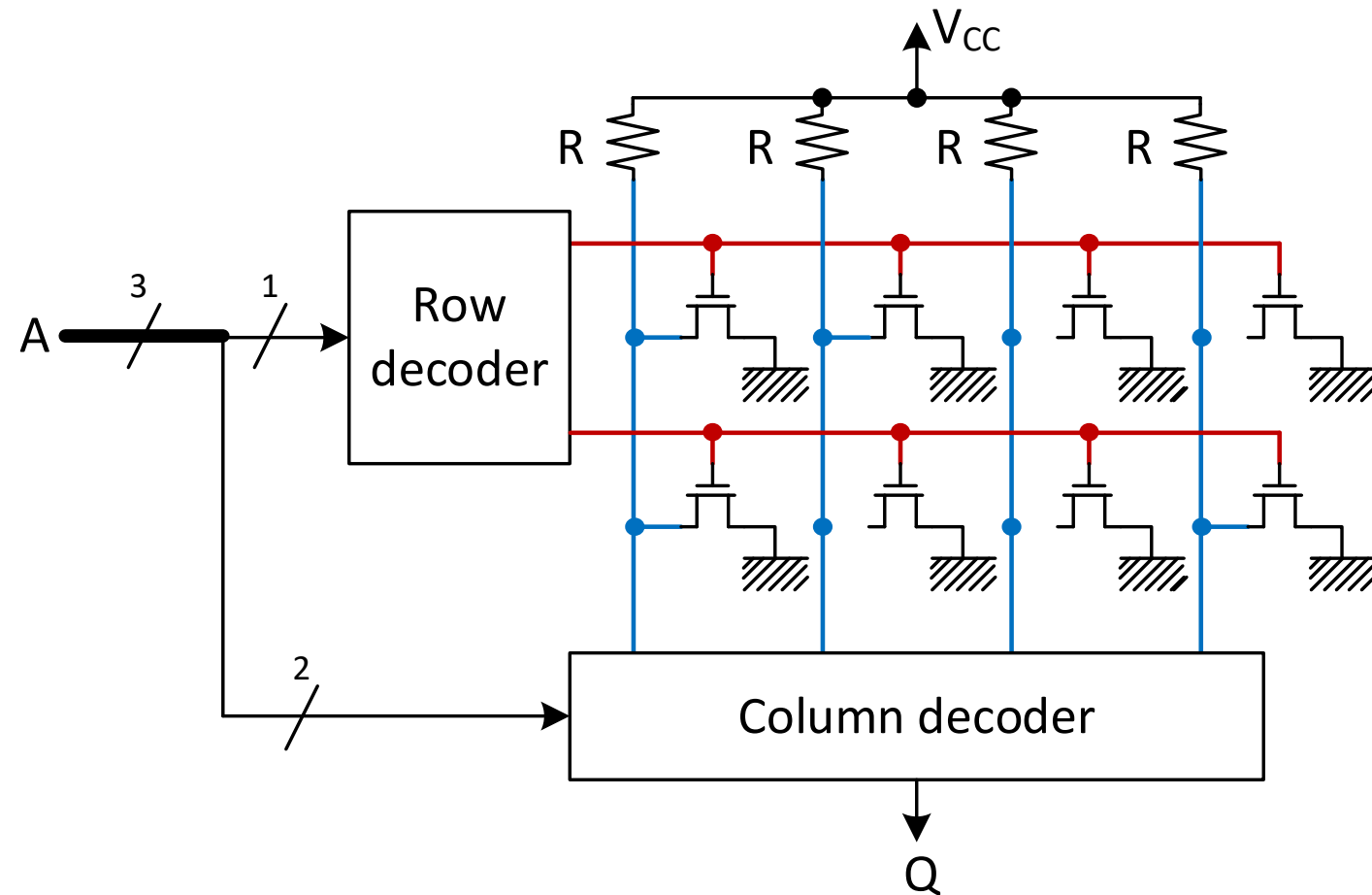

# PROM – Principle of operation

- Example
  - Reading cell (0,2)

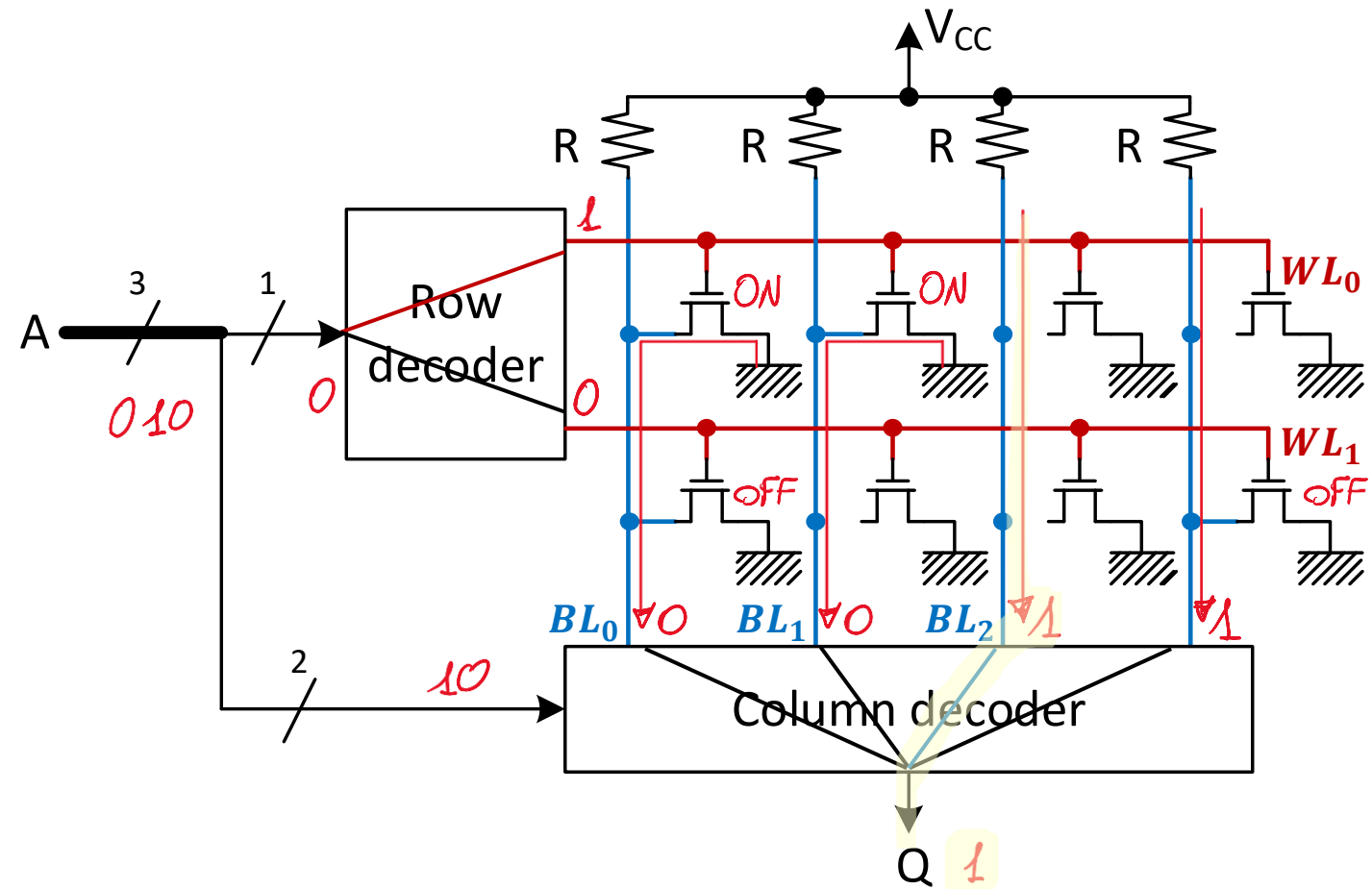



# PROM – Remarks and applications

- **Anti-fuses** can be used instead of fuses
  - Opposite of fuse
    - Default (not programmed) = open circuit
    - Programmed (with high current flow) = short circuit
- Early PROMs had reliability problems
  - Incompletely vaporized fuses
  - Floating shrapnel inside the IC package
- Target applications
  - The same as mask-ROMs



Thank you for your attention

Luca Crocetti  
([luca.crocetti@unipi.it](mailto:luca.crocetti@unipi.it))