



Electronics Systems (938II)

Lecture 1.1


Modern Electronic Systems (intro) – Design flow and HDL

Brief recall on CMOS technologies

- Digital electronics systems
 - Different technologies

Brief recall on CMOS technologies

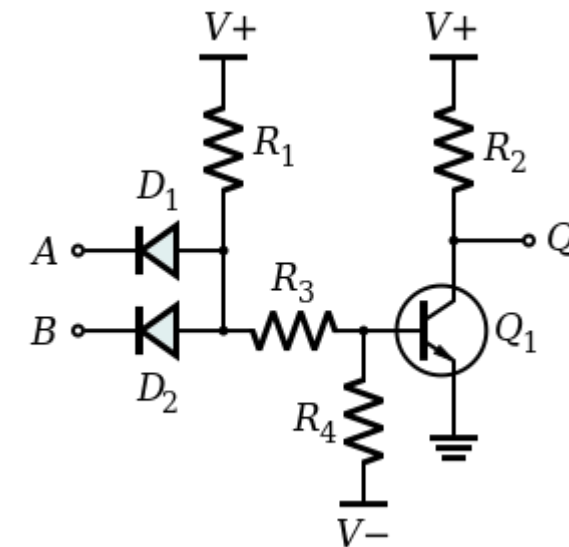
- Digital electronics systems
 - Different technological families
 - DTL = Diode-Transistor Logic



NAND gate

Brief recall on CMOS technologies

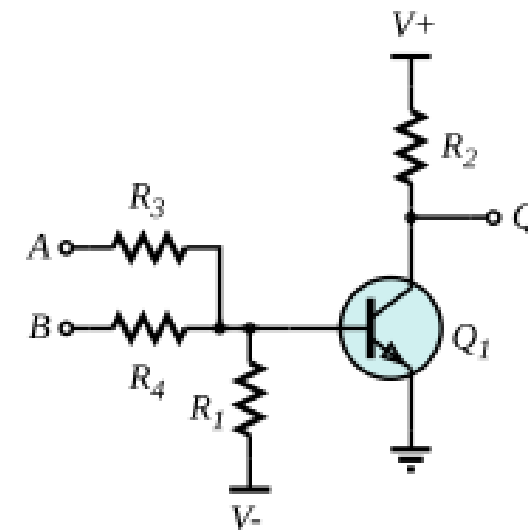
- Digital electronics systems
 - Different technological families
 - DTL
 - RTL = Resistor-Transistor Logic



NOR gate

Brief recall on CMOS technologies

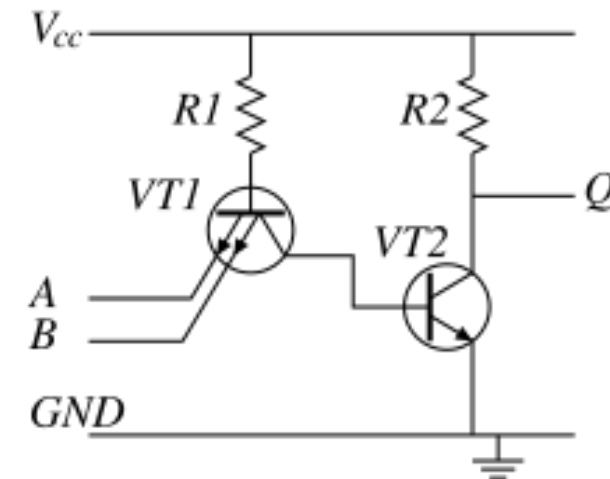
- Digital electronics systems
 - Different technological families
 - DTL
 - RTL
 - TTL = Transistor-transistor Logic



NAND gate

Brief recall on CMOS technologies

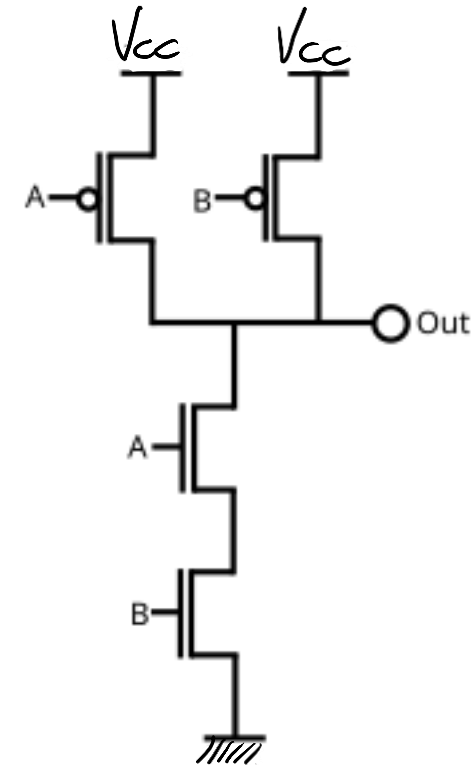- Digital electronics systems
 - Different technological families
 - DTL
 - RTL
 - TTL
 - CMOS = Complementary MOS (logic)
 - p-MOS
 - n-MOS



NAND gate

Brief recall on CMOS technologies

- Digital electronics systems
 - Different technological families
 - DTL
 - RTL
 - TTL
 - **CMOS**




Dominant technology:

- Very Large Scale Integration (VLSI)
- Complete system on unique chip
 - Sensor
 - ADC
 - Digital logic

Integration Scale and VLSI circuits

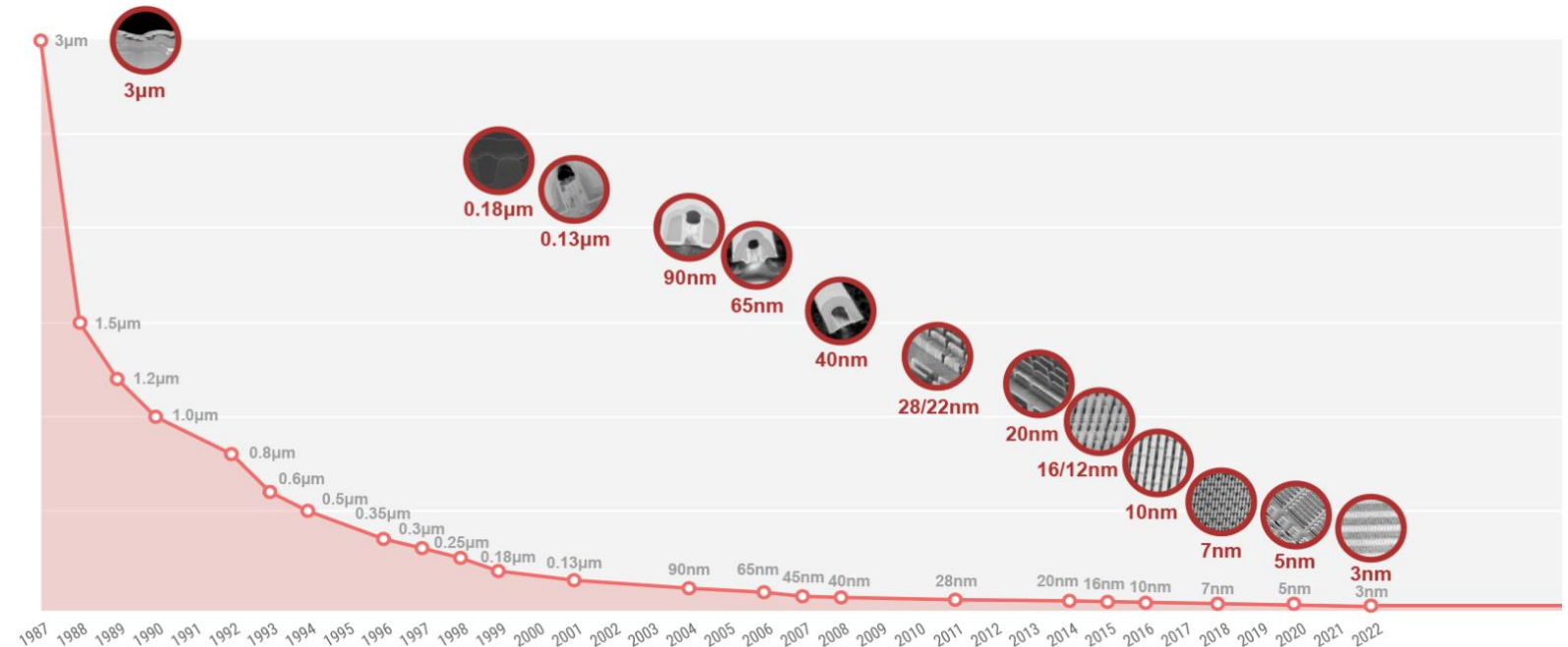- Extreme miniaturization supported by CMOS technologies
 - From TSMC* website:




* TSMC = semiconductor manufacturer

Integration Scale and VLSI circuits

- Extreme miniaturization supported by CMOS technologies
 - Larger number of transistors for the same silicon area
 - Cost reduction: chip cost \propto silicon area
 - Lower supply voltage
 - Lower power consumption
 - Higher frequencies
 - More compact logic gates \approx lower propagation delays


Integration Scale and VLSI circuits

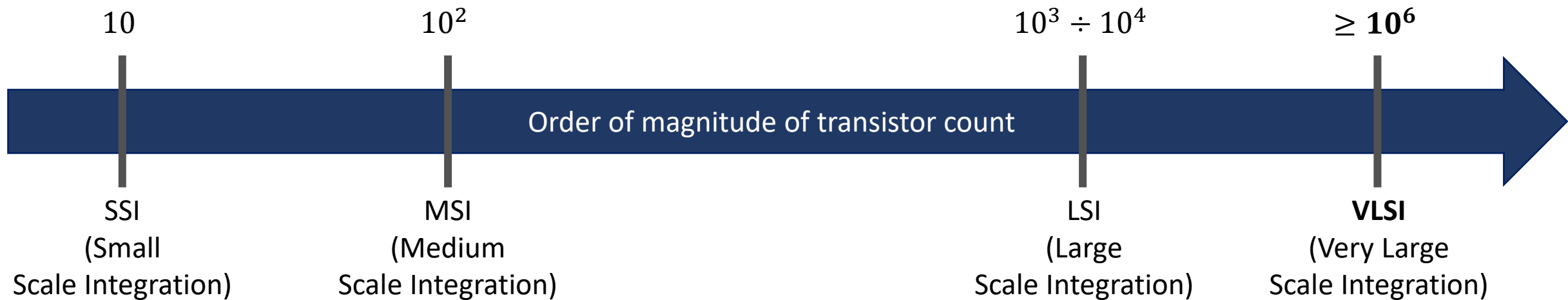- Number of transistors in the same chip
- Over the years, we passed
 - From SSI (Small Scale Integration): transistor count $\propto 10$
 - To **VLSI** (Very Large Scale Integration): transistor count $\geq 10^6$



Integration Scale and VLSI circuits

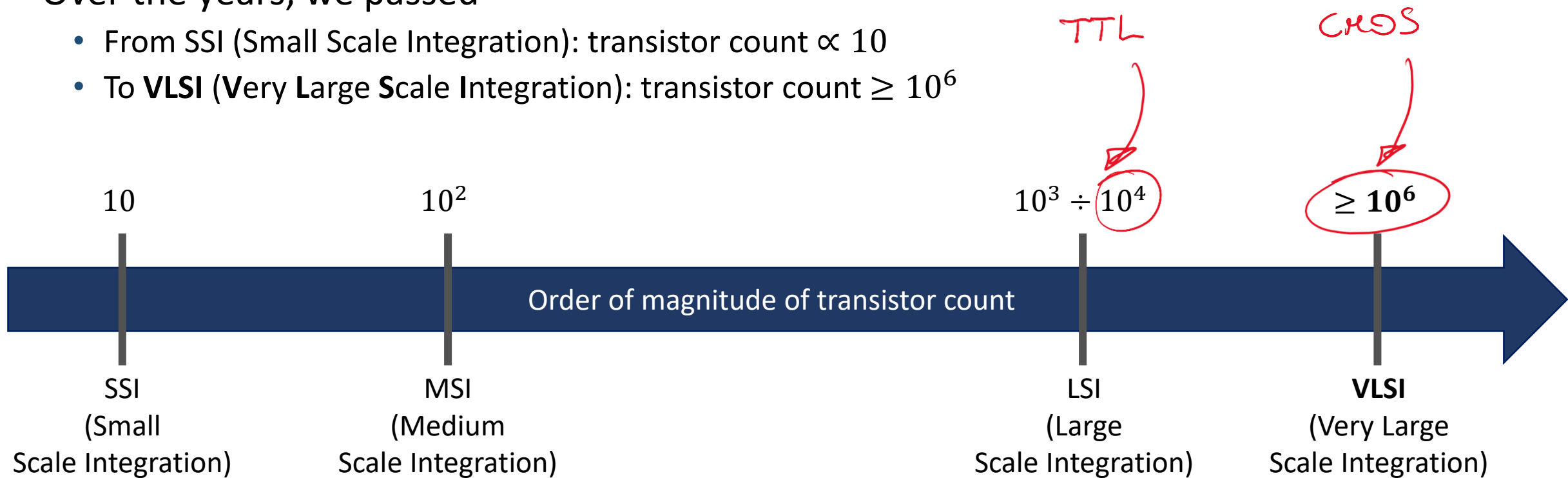
- Number of transistors in the same chip
- Over the years, we passed
 - From SSI (Small Scale Integration): transistor count $\propto 10$
 - To **VLSI** (Very Large Scale Integration): transistor count $\geq 10^6$




Integration Scale and VLSI circuits

- In other words, we passed ...

... from this, ...

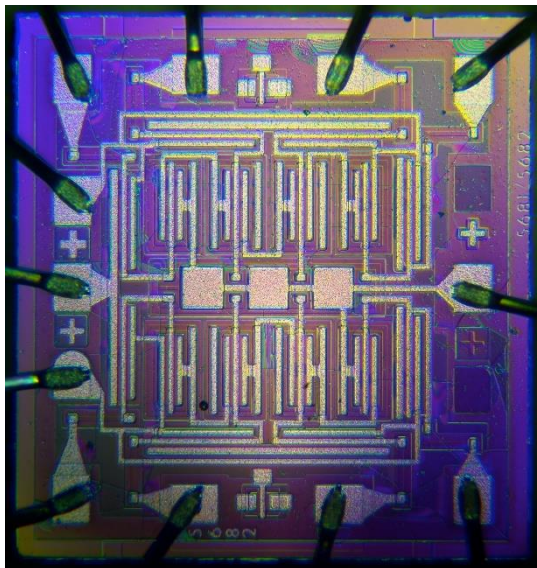


... to this!

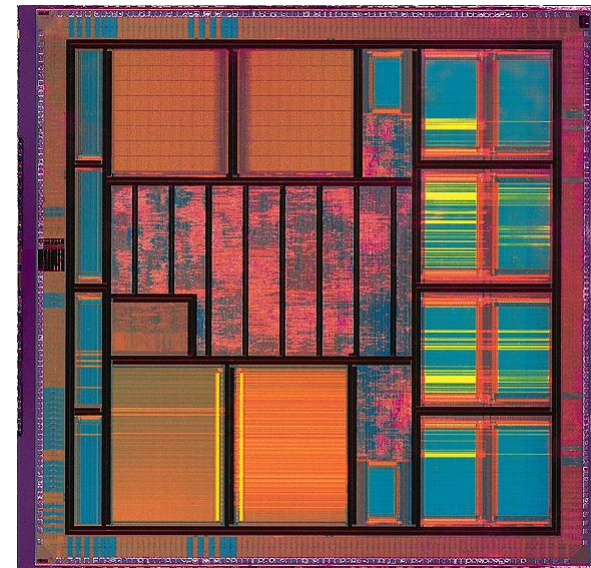


Integration Scale and VLSI circuits

- In other words, we passed ...

... from this, ...

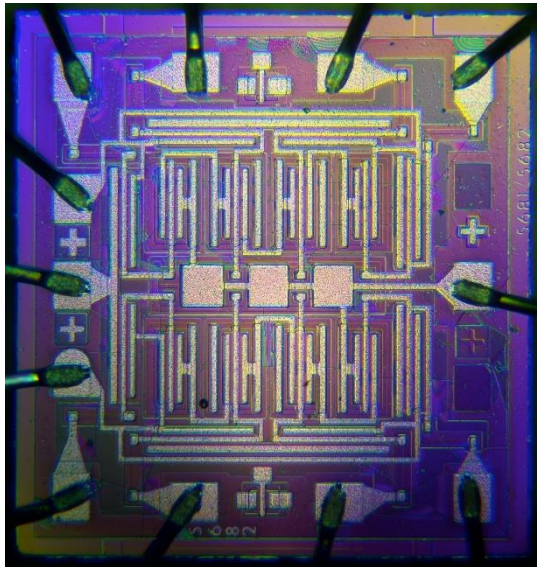

... to this!

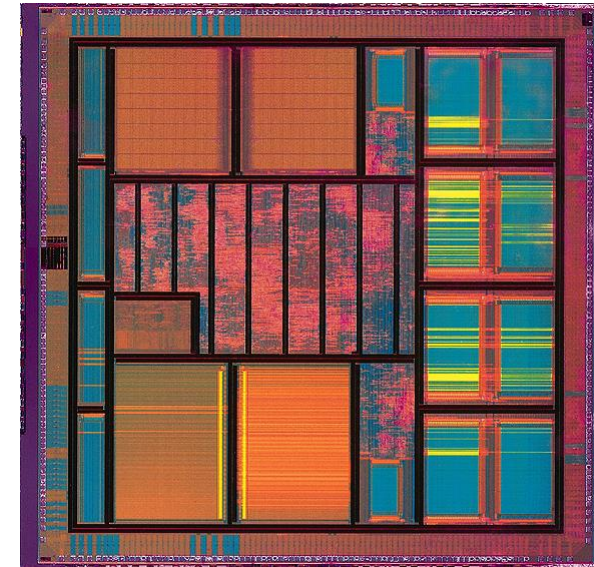


Layout of a modern Intel processor

Integration Scale and VLSI circuits

- In other words, we passed ...


... from this, ...

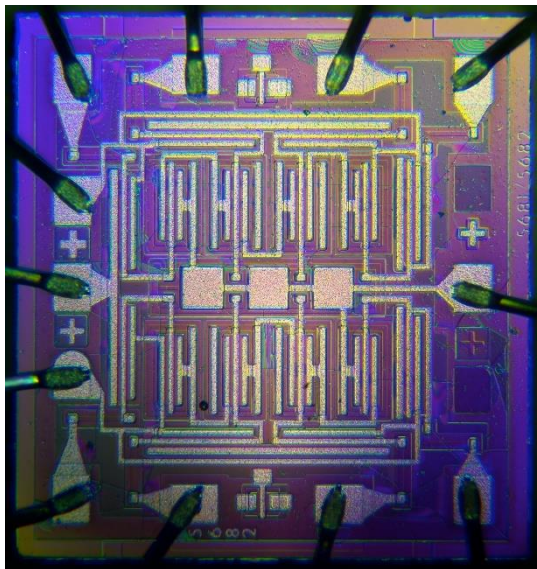

Hand design



... to this!

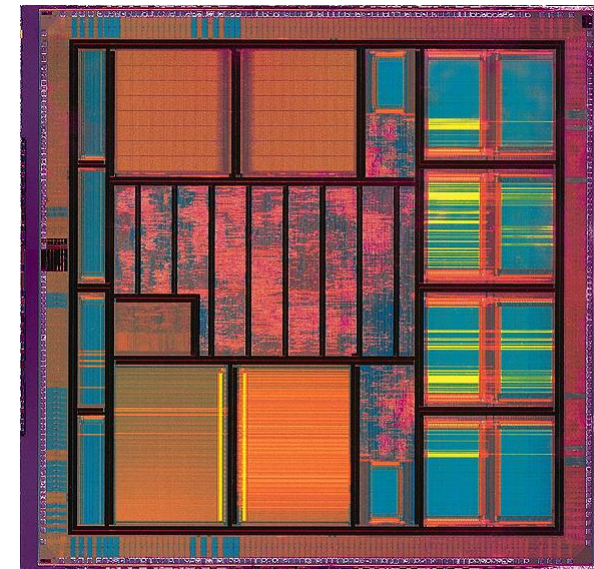

Automated design!!!

VLSI circuits


- Most modern digital electronic systems (or the digital part of an analog and digital system) are ...
 - ... VLSI circuits
 - ... based on CMOS technologies
 - ... designed using automated tools
 - EDA = Electronic Design Automation

VLSI circuits


- Most modern digital electronic systems (or the digital part of an analog and digital system) are ...
 - ... VLSI circuits
 - ... based on CMOS technologies
 - ... designed using **automated tools**
 - **EDA** = Electronic Design Automation

HDL for design of VLSI circuits

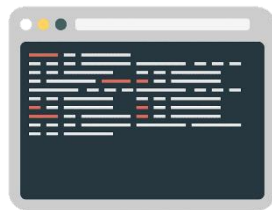- Automated design of modern digital circuits relies on the usage of **HDL** languages
 - HDL = Hardware Description Language
 - Languages (programming code) that describe a (digital) circuit




HDL code

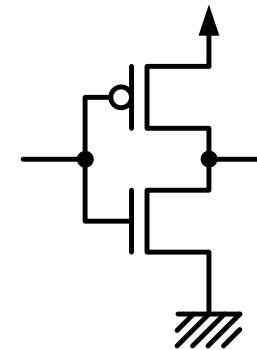

Corresponding circuit


HDL for design of VLSI circuits

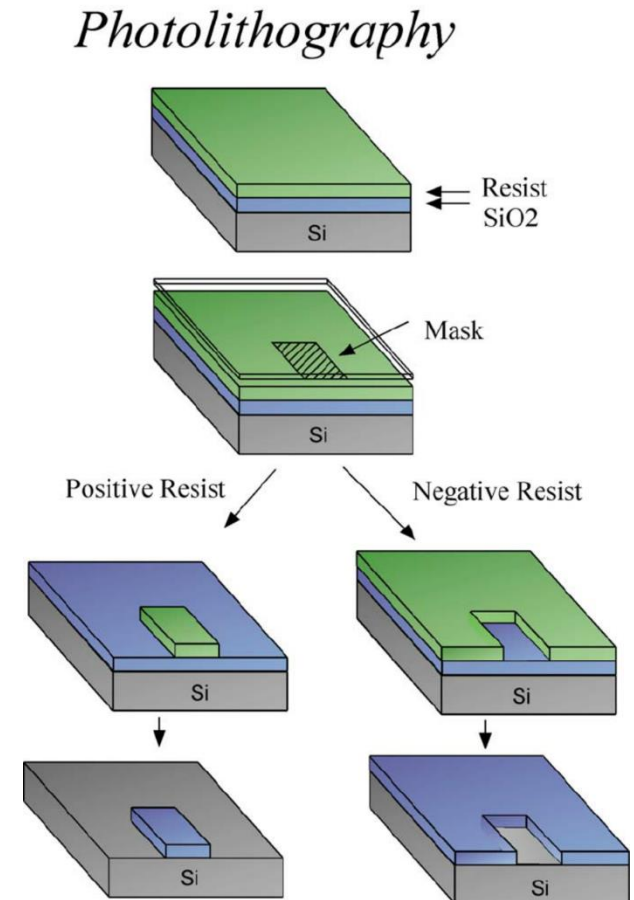- Design flow
 - HDL code → Layout of the circuit
- Circuits manufacturing
 - Photolithography
 - The circuit layout define the mask(s) used in the photolithographic process



HDL for design of VLSI circuits

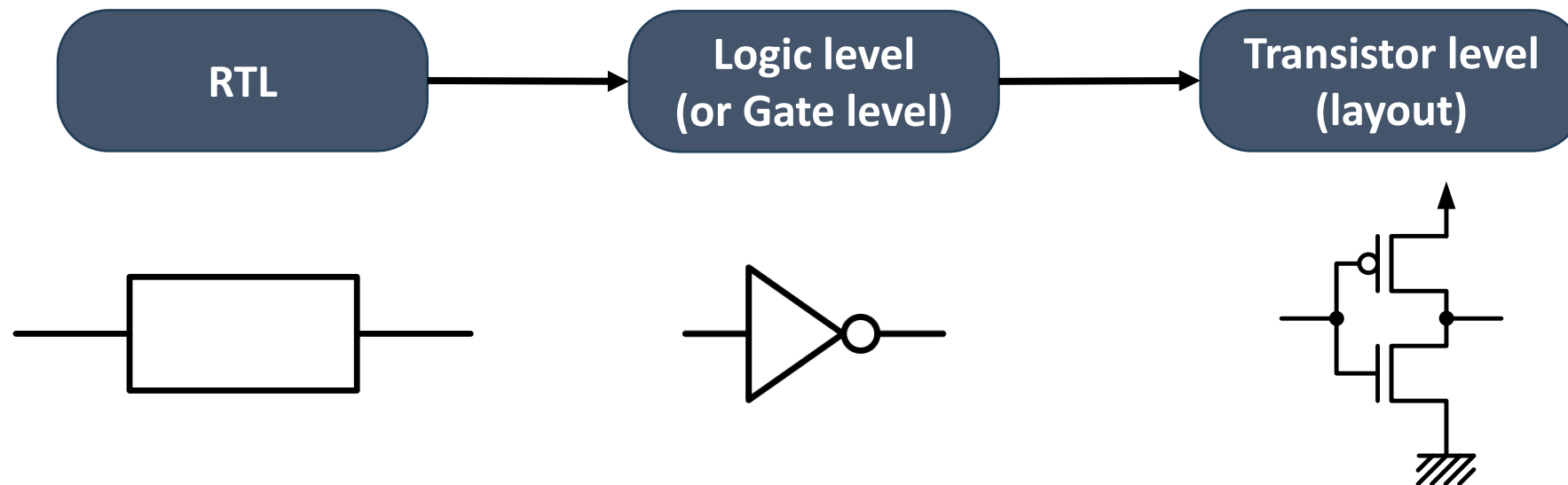- Design flow
 - HDL code → Layout of the circuit
 - 3 representation levels




HDL for design of VLSI circuits

- Design flow


- HDL code → Layout of the circuit
- 3 representation levels

RTL = Register Transfer Level

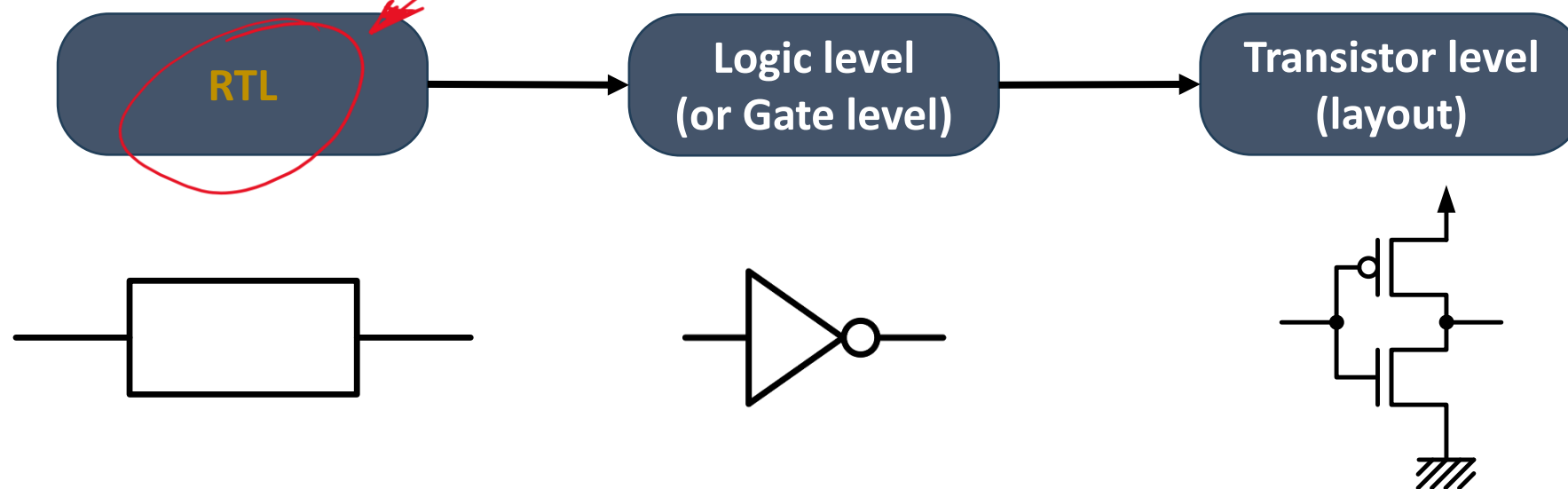


HDL for design of VLSI circuits

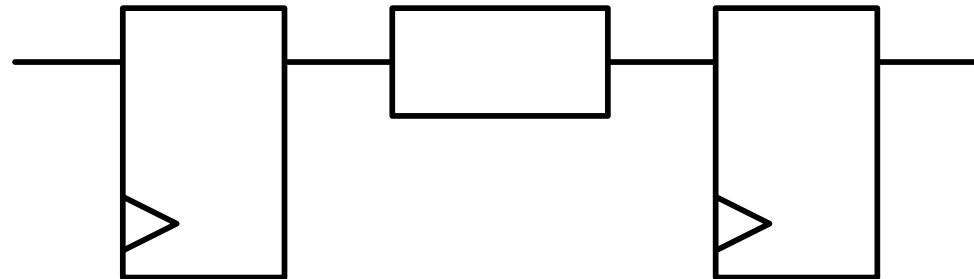- RTL
 - Abstract description/representation of the circuit in terms of
 - **Registers** (we are going to see registers later)
 - **Logical operation(s)** on the signals from registers




HDL for design of VLSI circuits

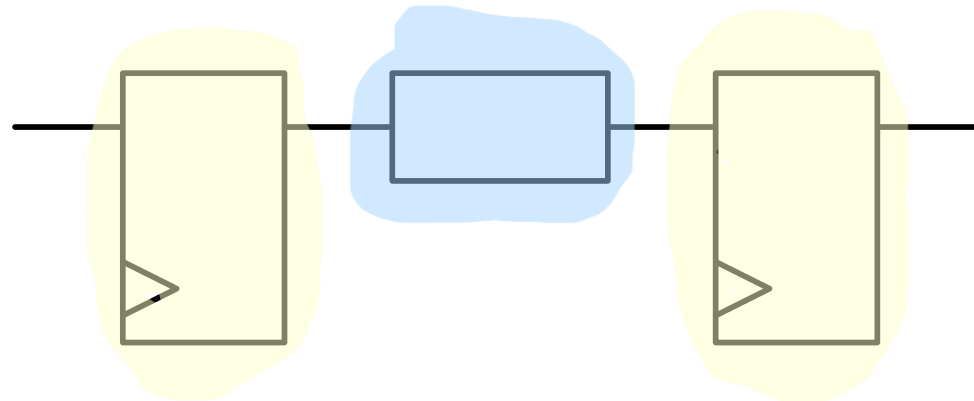- RTL
 - Abstract description/representation of the circuit in terms of
 - **Registers** (we are going to see registers later)
 - **Logical operation(s)** on the signals from registers



HDL for design of VLSI circuits

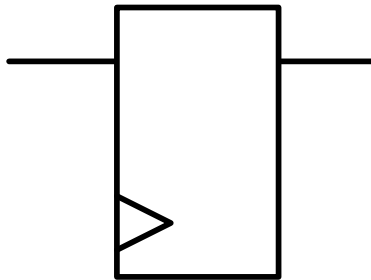- RTL
 - Representation of circuit components/elements: corresponding **functional symbol**




Functional symbol of
register



Functional symbol of
generic function

HDL for design of VLSI circuits

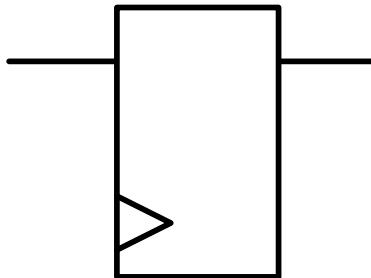- RTL
 - Representation of circuit components/elements: corresponding **functional symbol**



Functional symbol of
register




Functional symbol of
generic function


- For functions/operations
 - The symbol may change depending on the operation it performs
 - For high-complexity functions, a generic box with an appropriate number of input(s) and output(s) is generally used
 - For single-gate functions (e.g., NOT, AND, NAND, OR, NOR, ...), the functional symbol correspond to the gate-level symbol

HDL for design of VLSI circuits

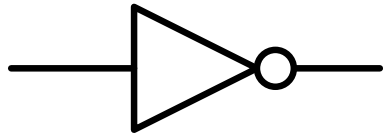- RTL
 - Representation of circuit components/elements: corresponding **functional symbol**
 - Examples of single-gate logical functions: **NOT**




(functional symbol – RTL)

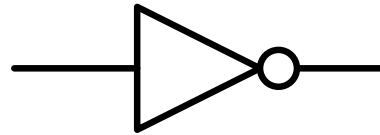


(gate-level)

HDL for design of VLSI circuits

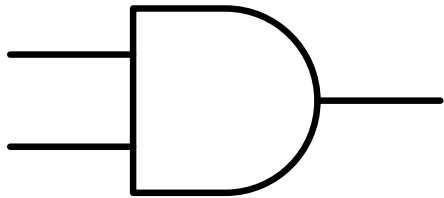- RTL
 - Representation of circuit components/elements: corresponding **functional symbol**
 - Examples of single-gate logical functions: **AND**




(functional symbol – RTL)

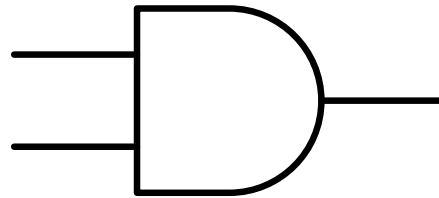


(gate-level)

HDL for design of VLSI circuits

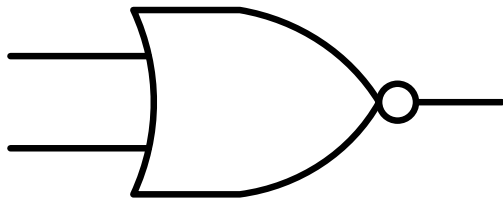- RTL
 - Representation of circuit components/elements: corresponding **functional symbol**
 - Examples of single-gate logical functions: **NOR**





(functional symbol – RTL)

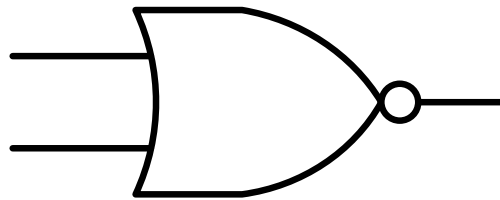


(gate-level)

HDL for design of VLSI circuits

- RTL
 - Examples

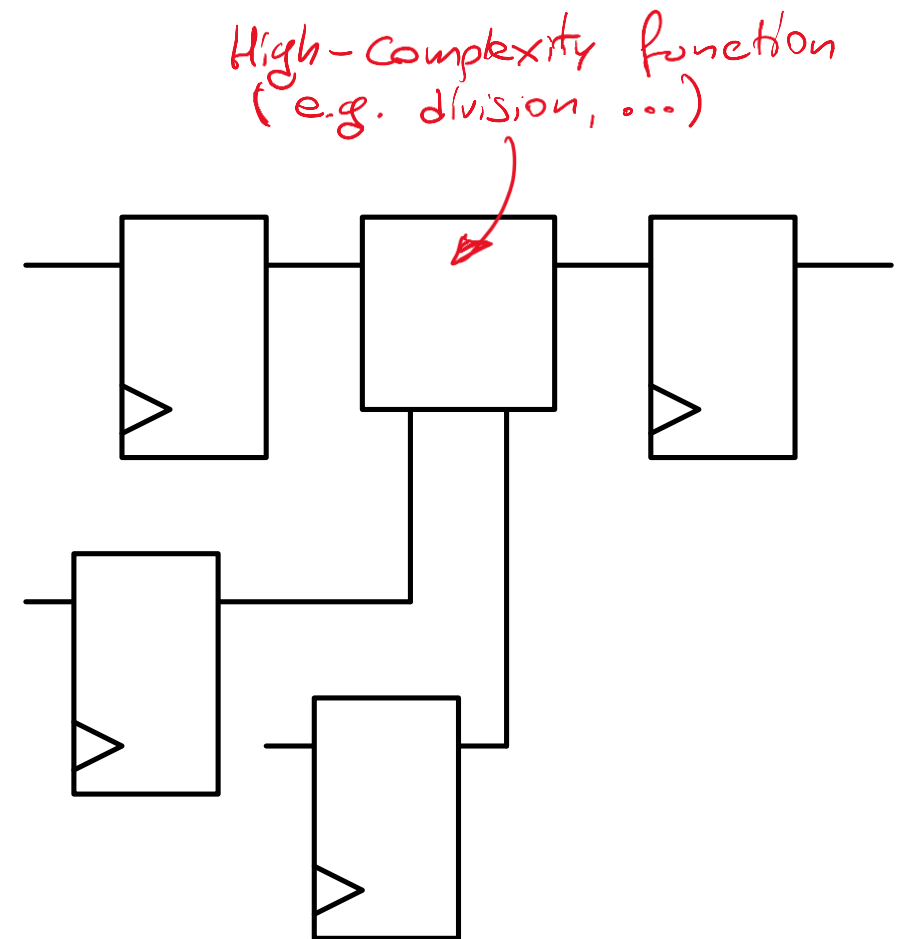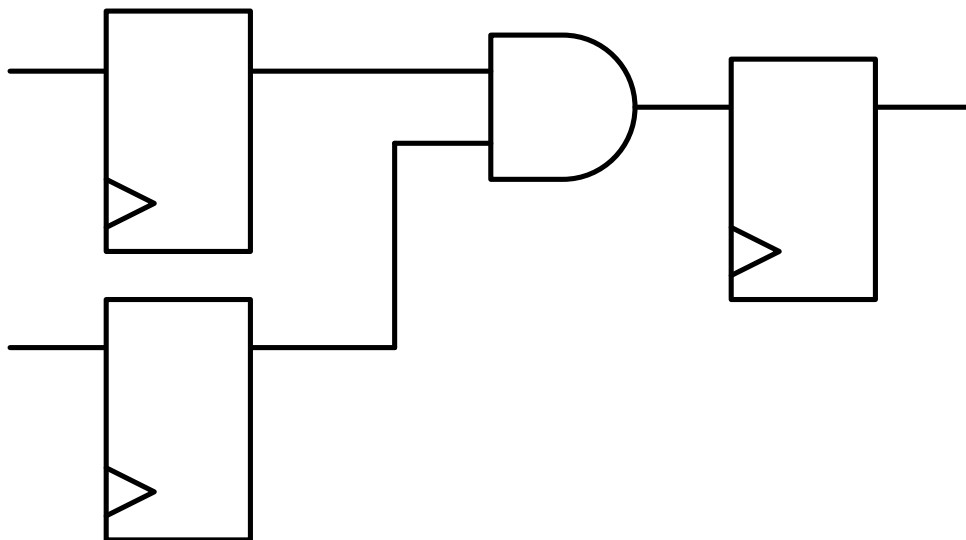


Brief recall on CMOS technologies

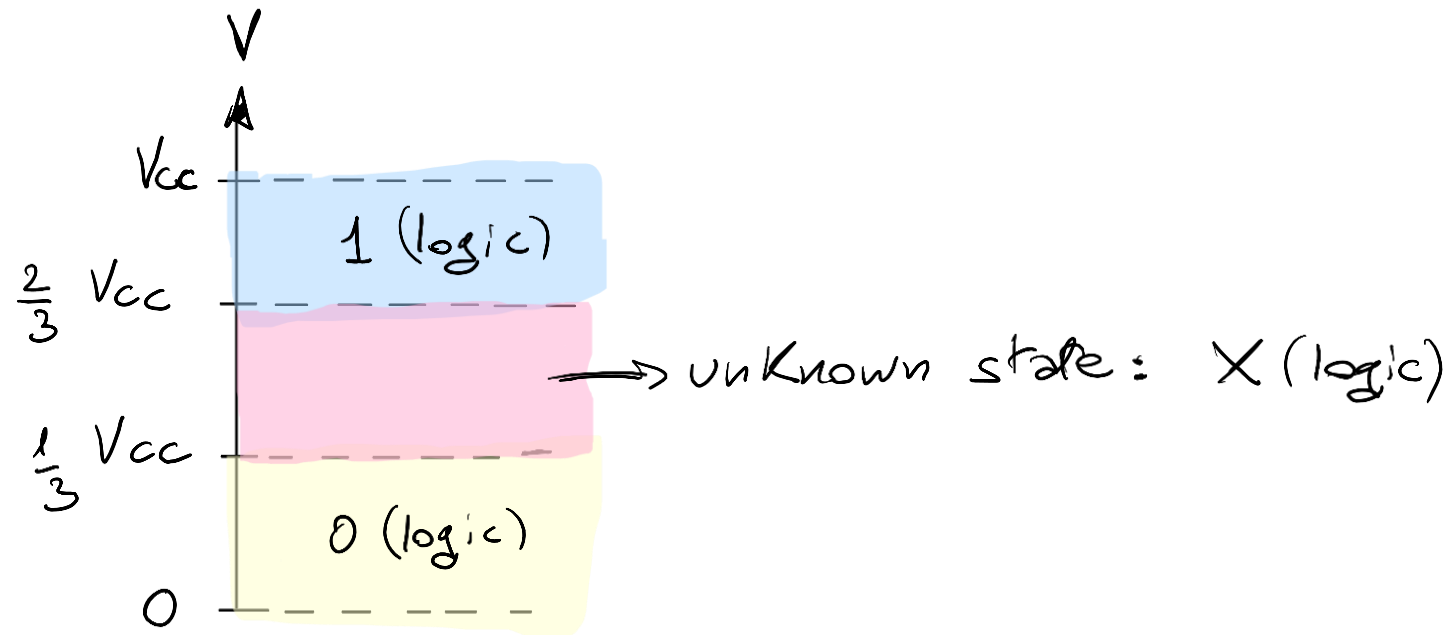

- Over the years, V_{CC} scaled from 5 V down to 0.9 V


Brief recall on CMOS technologies

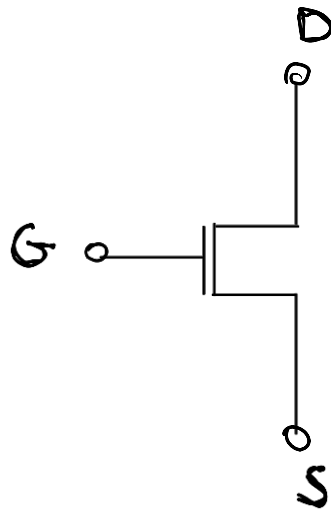- n-MOS transistor \approx controlled switch




Brief recall on CMOS technologies

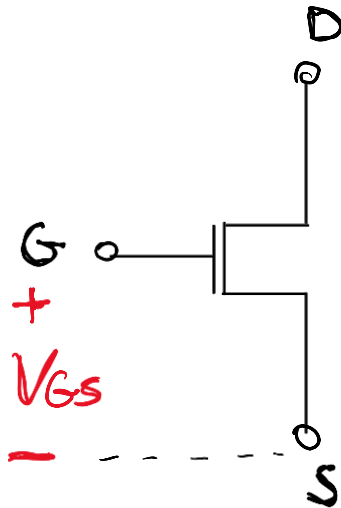- n-MOS transistor \approx controlled switch




Brief recall on CMOS technologies

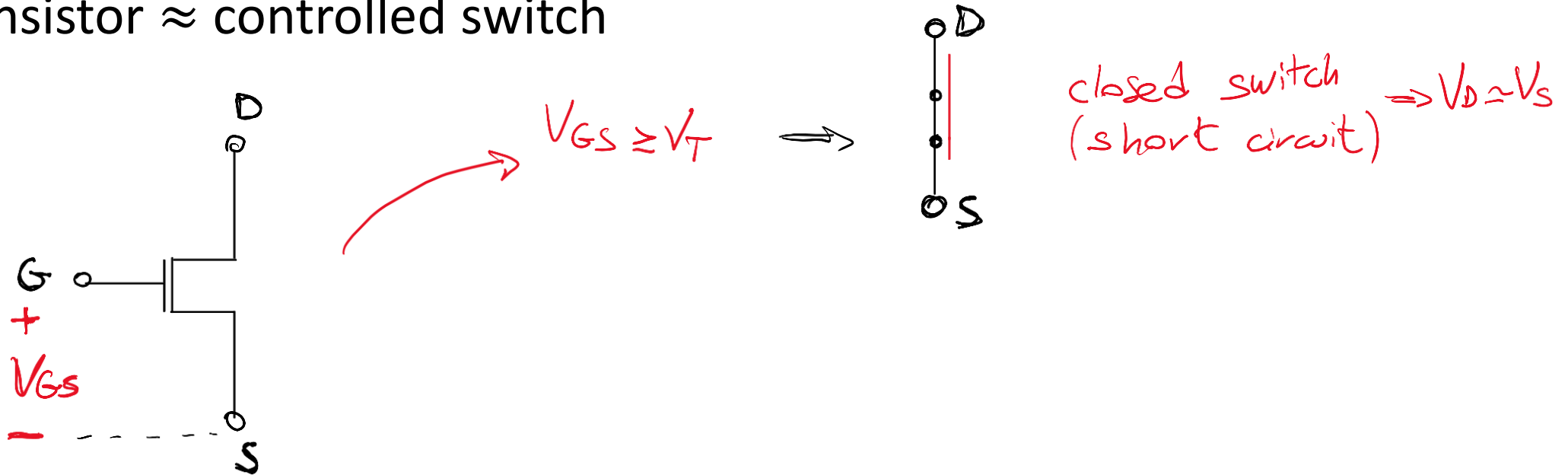- n-MOS transistor \approx controlled switch




Brief recall on CMOS technologies

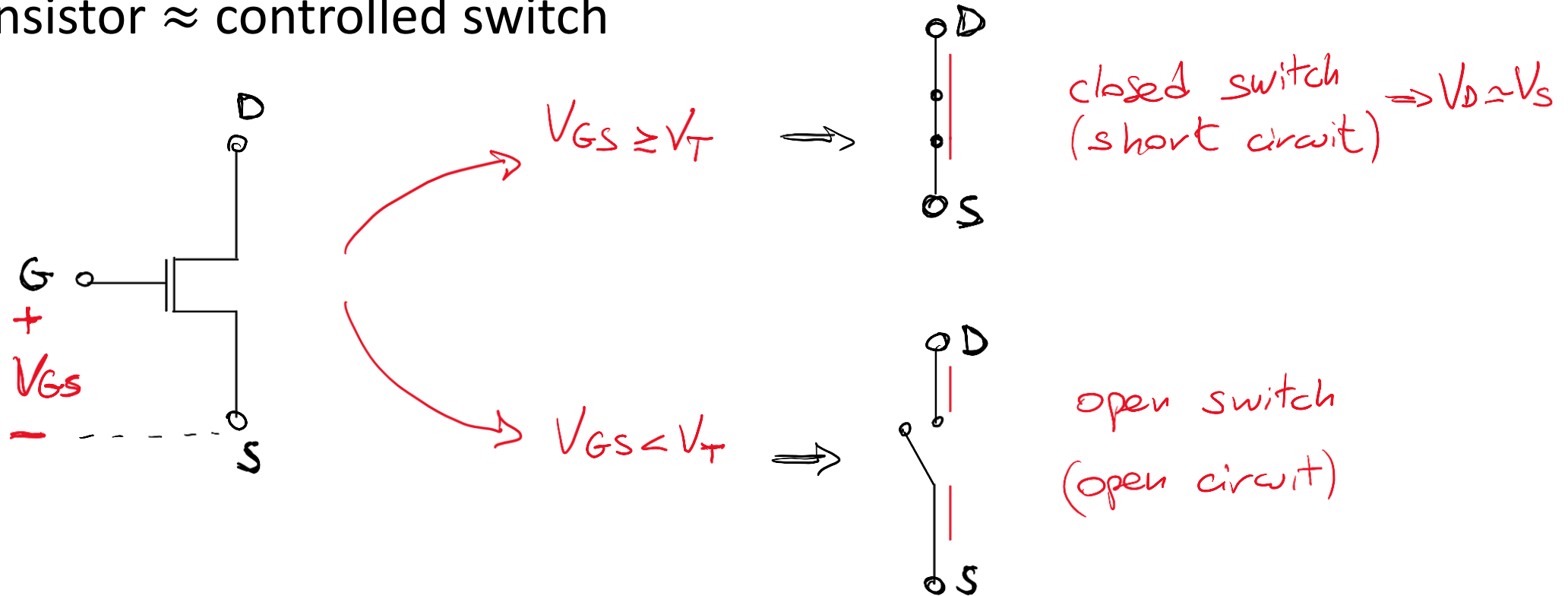- n-MOS transistor \approx controlled switch



Brief recall on CMOS technologies

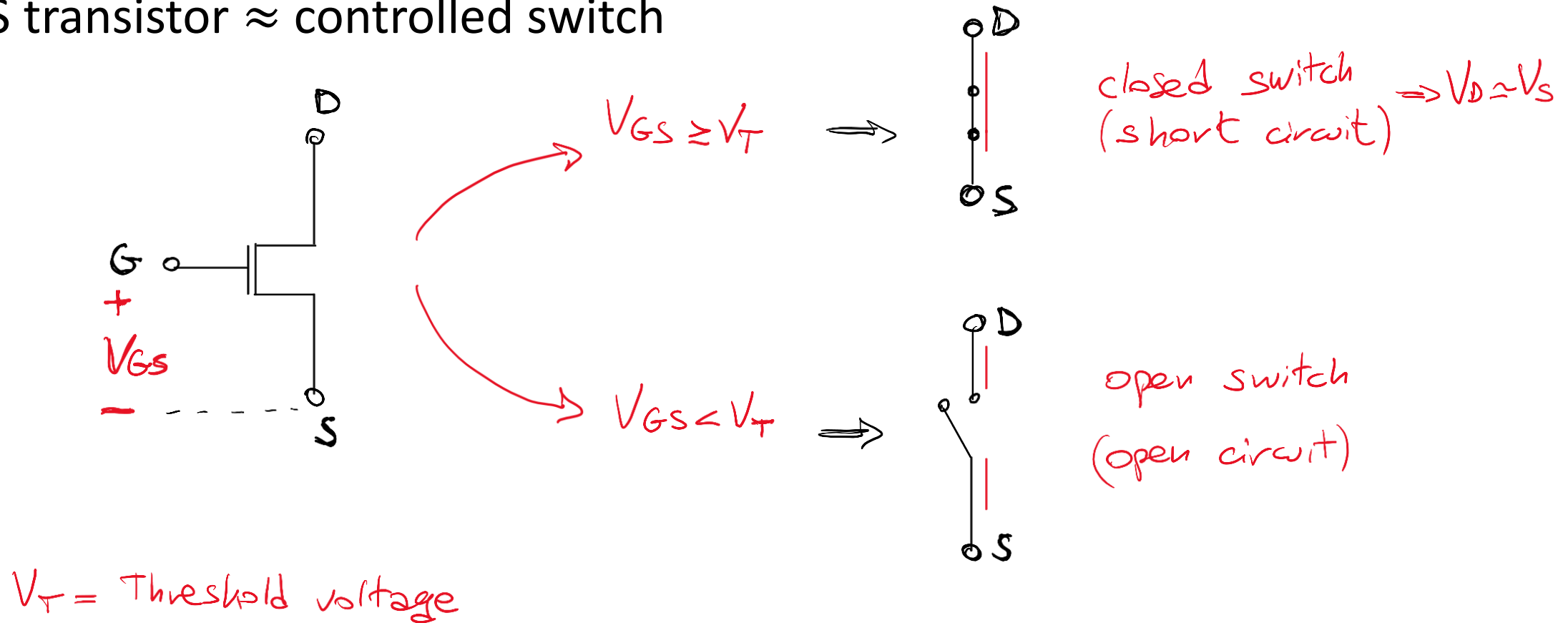- n-MOS transistor \approx controlled switch




Brief recall on CMOS technologies

- In CMOS circuits
 - V_{CC} is the supply voltage $\rightarrow V_{CC}$ is the maximum voltage applied to all parts of the circuit
 - At least during the operation of the circuit
 - Some exceptions (e.g., programming, ...): will be clearer later
 - **Always: $V_{CC} \geq V_T$**
 - **Always: $0V < V_T$**


Brief recall on CMOS technologies

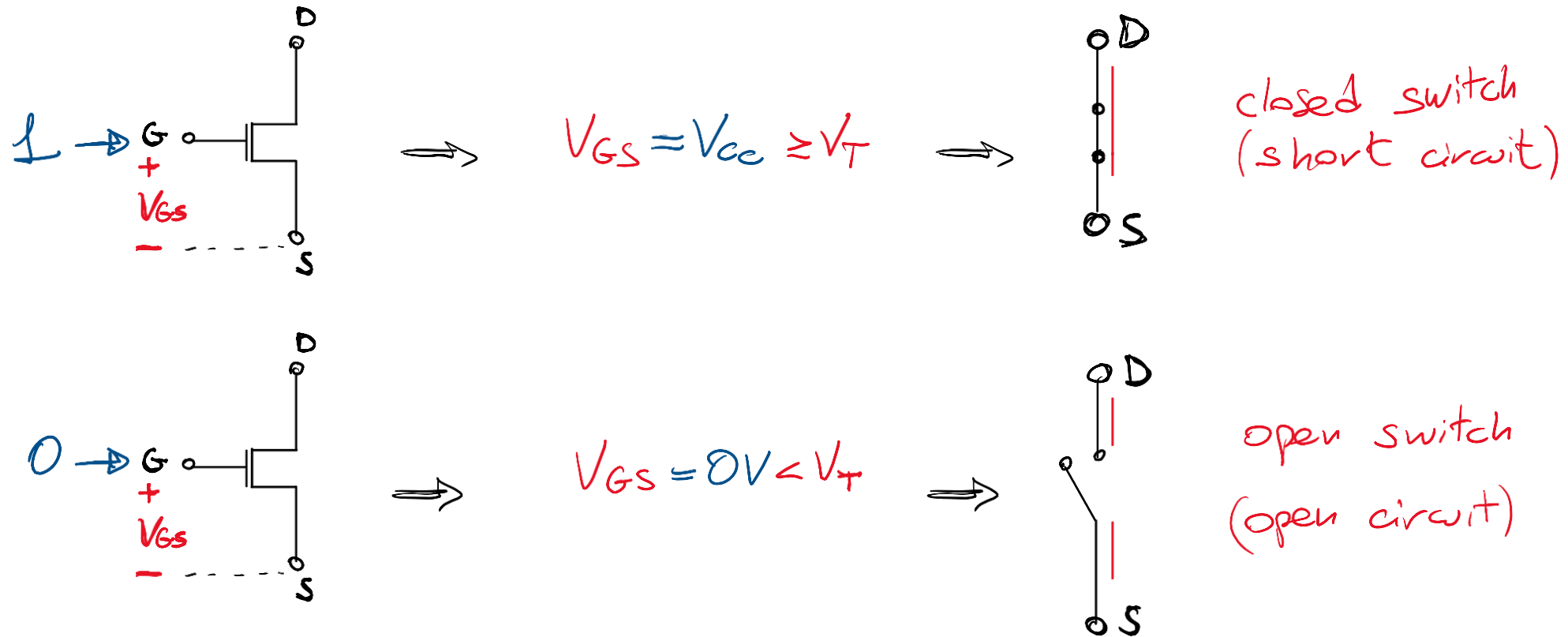- n-MOS transistor \approx controlled switch



Brief recall on CMOS technologies

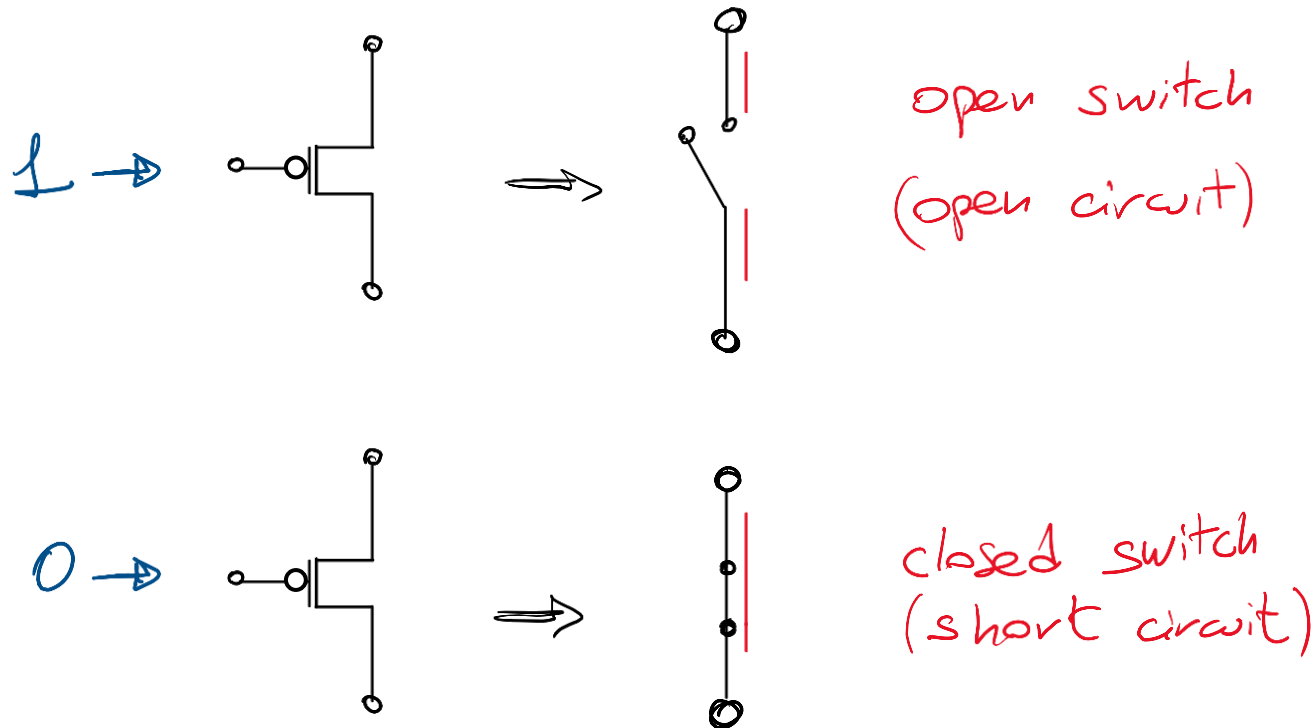- p-MOS transistor \approx controlled switch (**dual of n-MOS**)





Brief recall on CMOS technologies

- Active-low signals
 - Definition
 - When 1, the (active-low) signal is disabled
 - When 0, the (active-low) signal is enabled

Brief recall on CMOS technologies

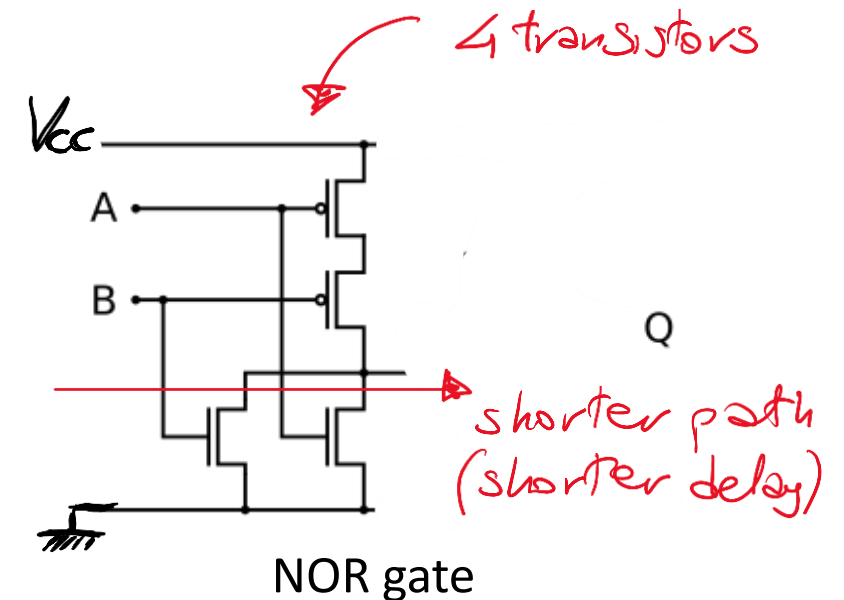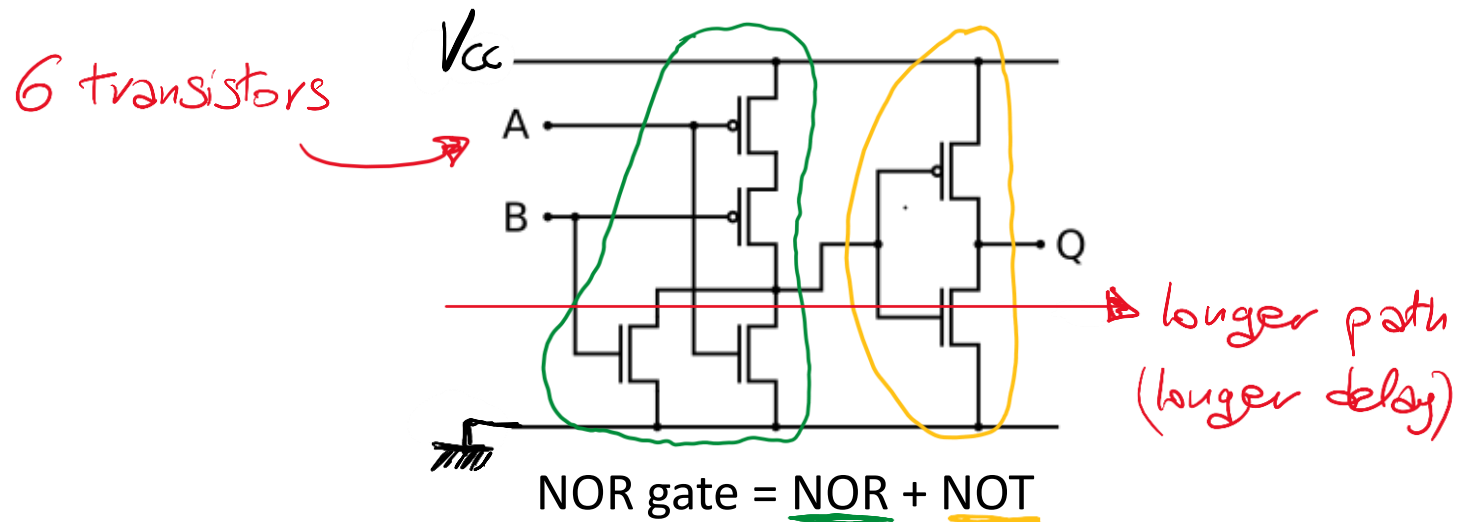- Active-low signals
 - Why?
 - Active-low signals can
 - Reduce the gate count (so the costs)
 - Improve the circuit “speed” (reduce the delay)





Thank you for your attention

Luca Crocetti
(luca.crocetti@unipi.it)